
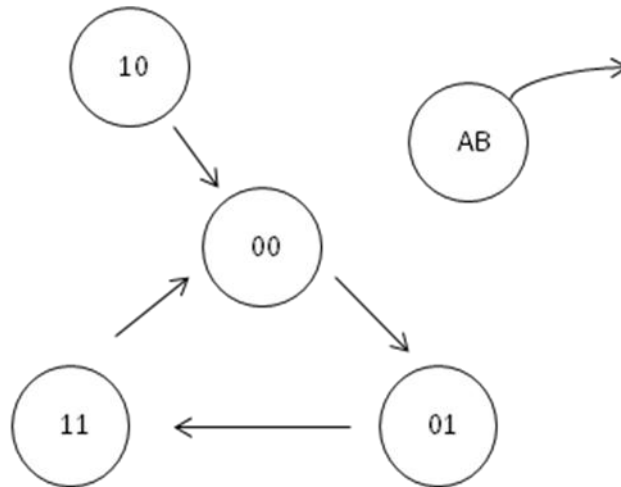


Exercise 5

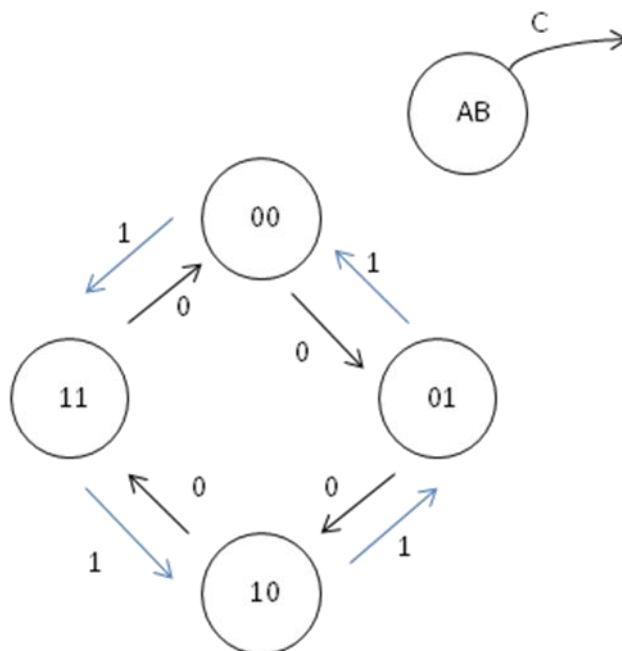1. Design a sequential circuit that satisfies the following state diagram.
 - a. By using D flip flops.
 - b. By using JK flip flops.



2. Design a sequential circuit that satisfies the following state diagram.
 - a. By using D flip flops.
 - b. By using JK flip flops.



-

