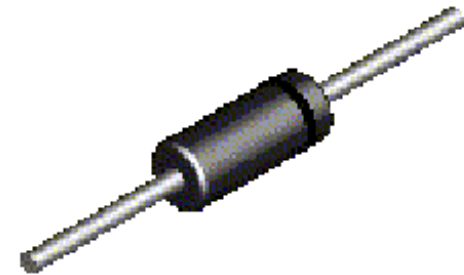


# Active Circuits

- Diodes
- BJT transistors, DC operation
- FET transistors, DC operation
- Operational amplifiers
- Power semiconductors

# Diodes

- Normal (silicon) diode
- Zener diode
- Schottky diode
- Capacitance diode
- LED
- Photodiode






DO-35



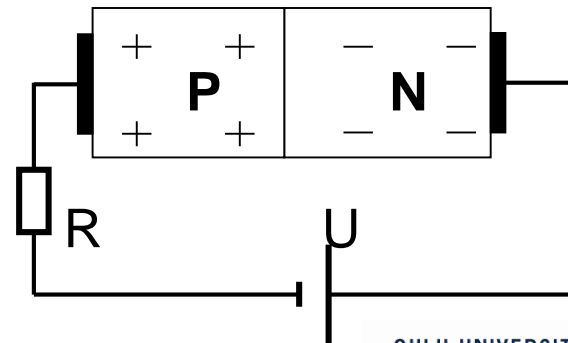
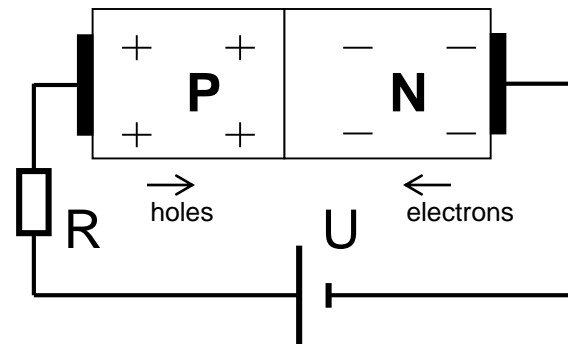
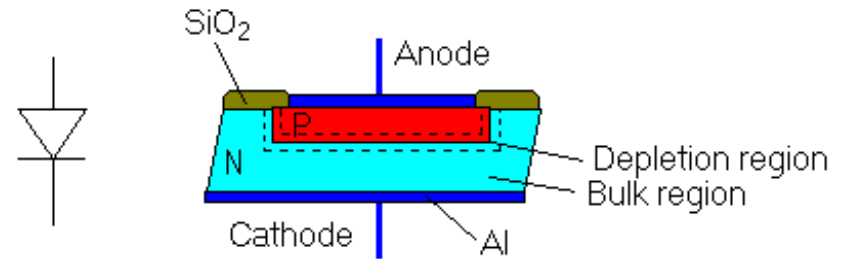
## Basic Operation

- When forward biased more electrons come from the supply to n region and more holes come from the supply
- This means continuous current flow
- Voltage across well-conducting silicon diode is about 0.7V



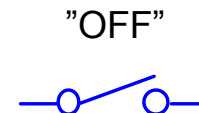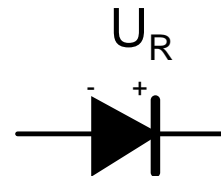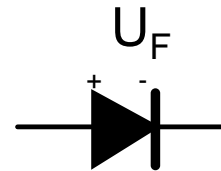
## An Ideal Diode

- A forward-biased diode conducts (switch on)
- A reverse-biased diode doesn't conduct (switch off)
- On-resistance tends to zero
- Off-resistance tends to infinity


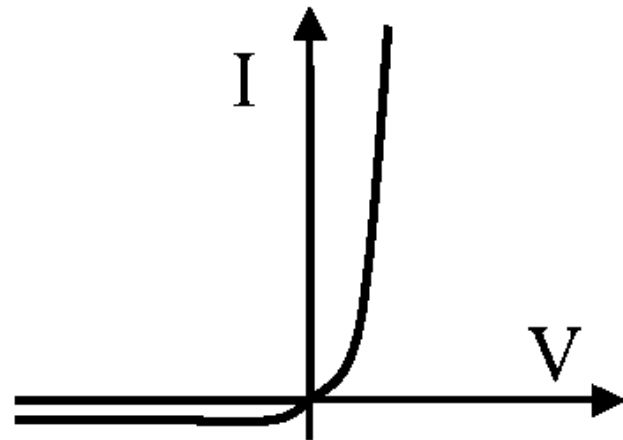
## A Real Diode

- In a real diode there is a certain voltage across a diode when it is forward-biased. This voltage is typically about 0.7V for normal silicon diode. In germanium and in Schottky diode this voltage is lower and in LED it is higher.



$$I_D = I_0 (e^{\frac{U_D}{U_T}} - 1)$$

$I_D$ =diode current


$U_D$ =diode voltage

$I_0$ =saturation current

$U_T = kT/q$  (25,2mV at room temperature)

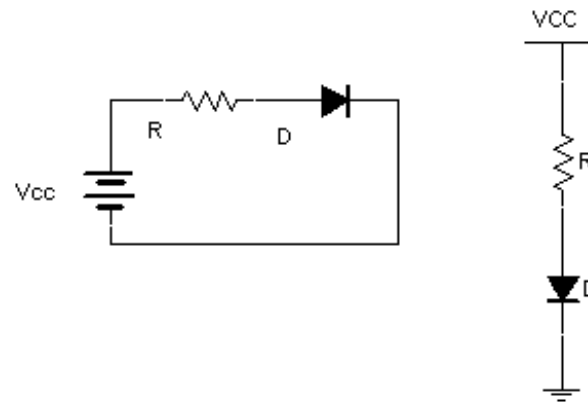
## A Forward-biased Diode

- When forward-biased a diode conducts very well. That's why a current limiting resistance is needed.
- Normally the value of the resistance is chosen according so that the current doesn't exceed the specified maximum ratings of a diode. Sometimes power dissipation requirements set the the value for the current limiting resistance.


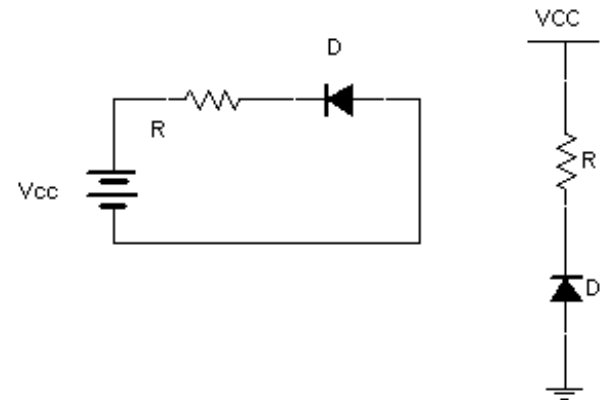
## A Reverse-biased Diode


When reverse-biased the current in a diode is very small. In a high-voltage environment you must check that you don't exceed the maximum reverse voltage across the diode. A break-down as unrecoverable.




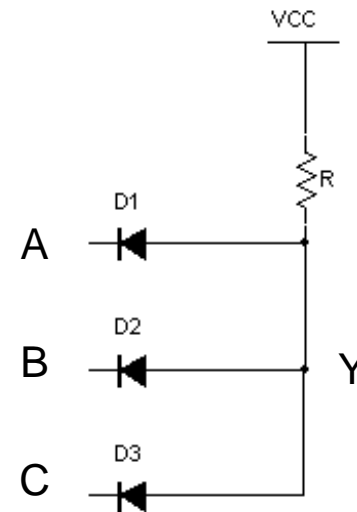
## Diode-based Logic Gate




- If some of the inputs is low, it means that output is also low
- If all the inputs are high the output is also high
- AND-gate







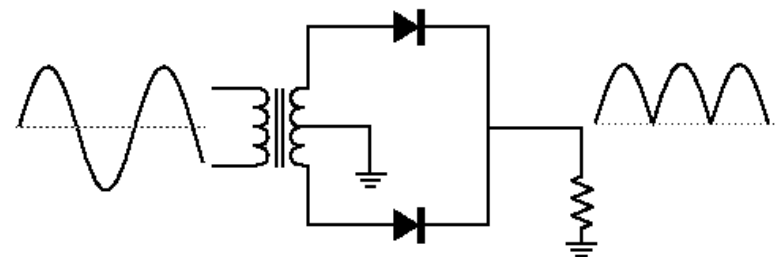
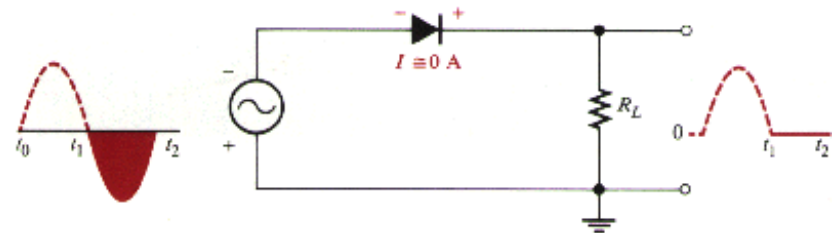
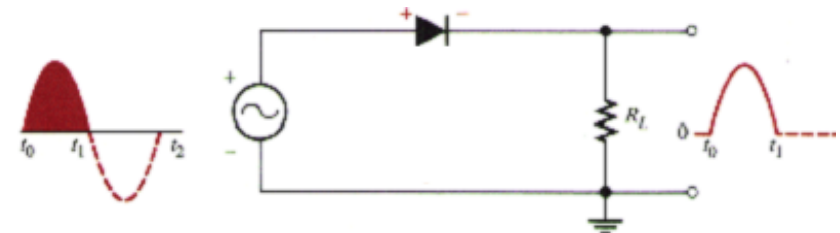
## Diode as a Rectifier

- Diode can be used to clip a part of the AC signal.
- In a half-wave rectifier a diode conducts during the positive half-cycle of the signal
- In a full-wave rectifier the negative half-cycle "is converted" to positive




## STUDY MATERIAL

# The Operation of a Bridge Rectifier

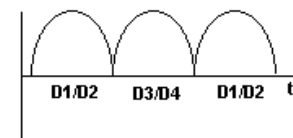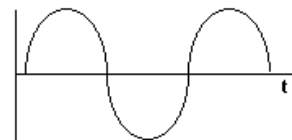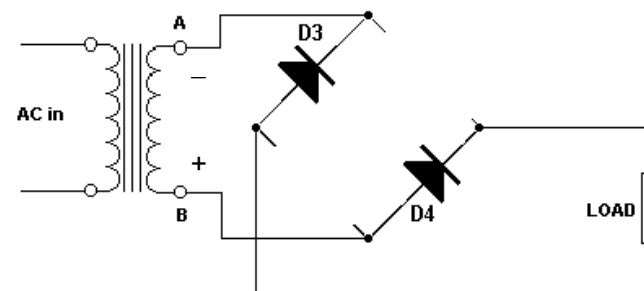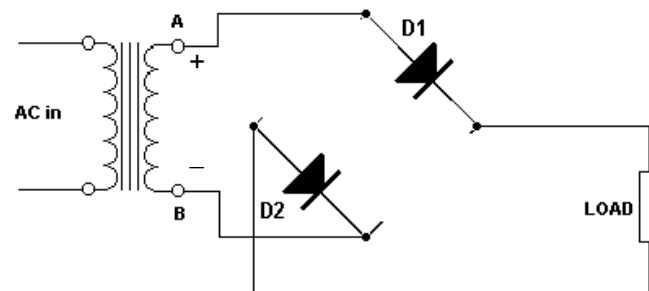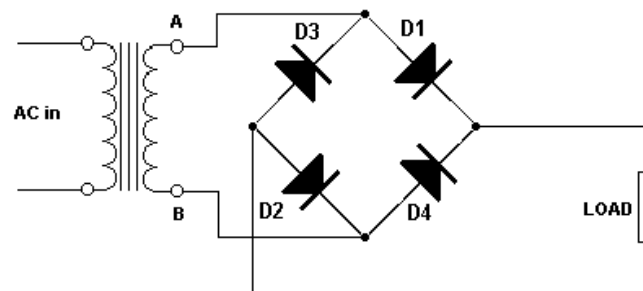



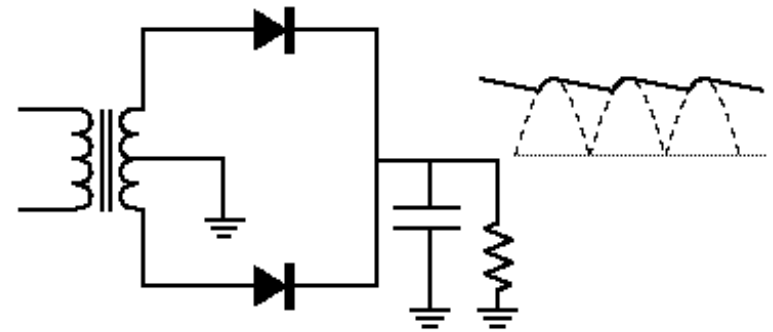
## DC Power Supply

- A transformer is needed to change the amplitude of an AC signal
- Diodes with tapped transformer form a full-wave rectifier
- A capacitor is used for filtering to reduce the ripple
- To improve this DC supply a fuse and a regulator could be added



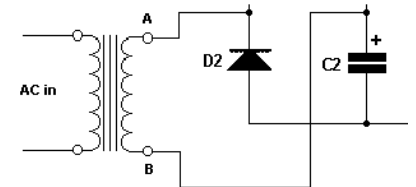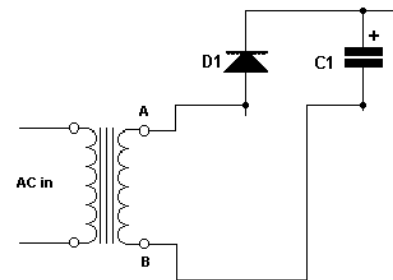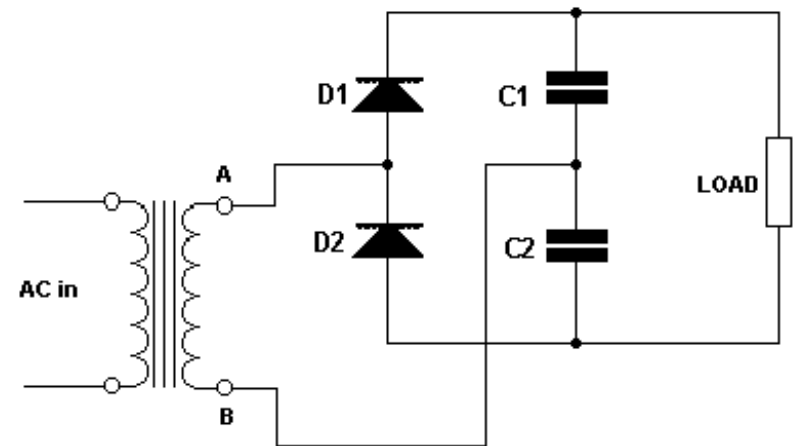
## Voltage Doubler

- During the positive half-cycle  $D_1$  conducts and  $C_1$  is charged
- During the negative half-cycle  $D_2$  conducts and  $C_2$  is charged
- Totally across  $C_1$  and  $C_2$  is twice the input amplitude



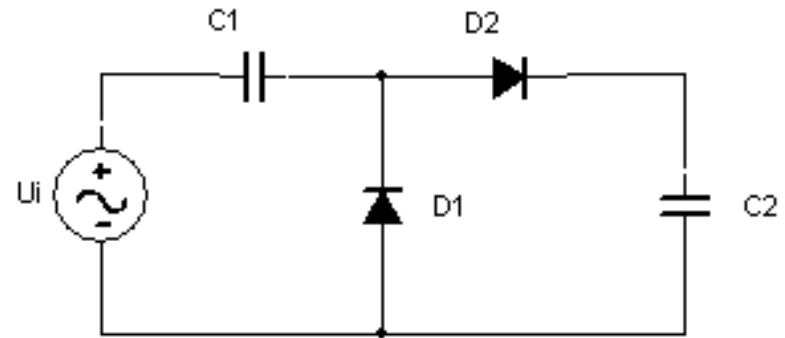
## Another Voltage Doubler

- During the negative half-cycle  $D_1$  conducts and  $C_1$  is charged
- During the positive half-cycle  $D_2$  conducts and  $C_2$  is charged with the voltage supplied from the generator plus charged in the  $C_1$  (during the negative half-cycle)




## Voltage Multiplier

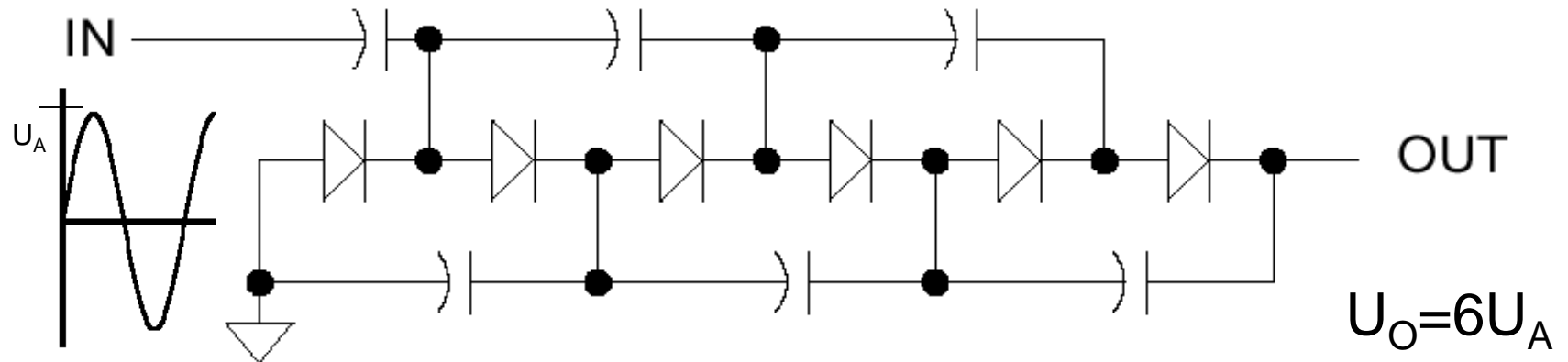
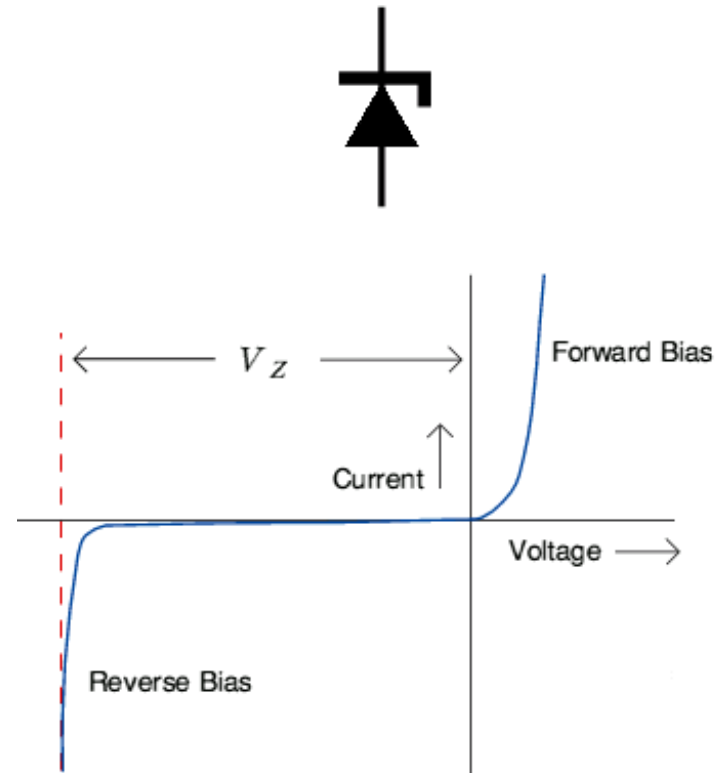
## Zener Diode



- When forward biased a Zener operates like a normal diode
- Zener (or avalanche) breakdown when reverse biased and Zener voltage reached
- Zener tolerates a breakdown unlike a normal diode





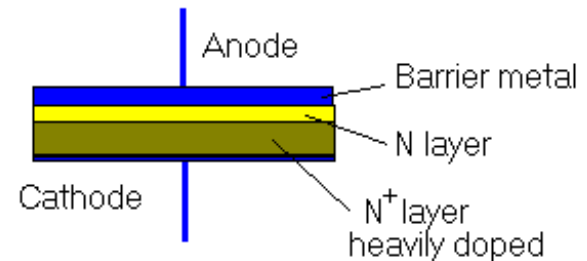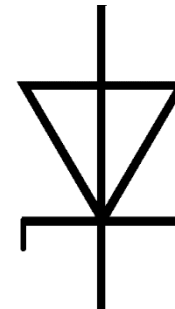
## Schottky Diode

- Schottky diode is a junction of metal and n type semiconductor material
- Schottky diode is faster than a normal diode.
- Also a forward voltage ( $U_F$ ) across Schottky diode smaller than in a normal diode



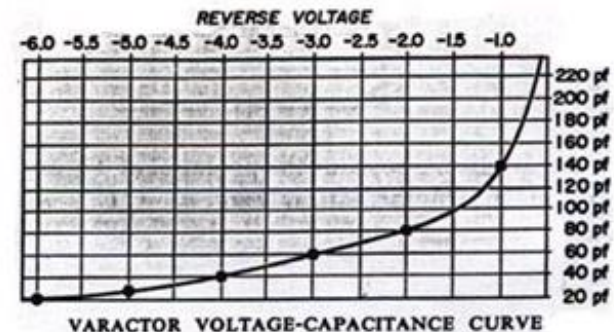
## Capacitance Diode (Varactor)

- The capacitance of the varactor can be changed by changing the reverse-biased voltage across the the varactor
- Used for example in voltage-controlled oscillators (VCXOs) for frequency adjusting



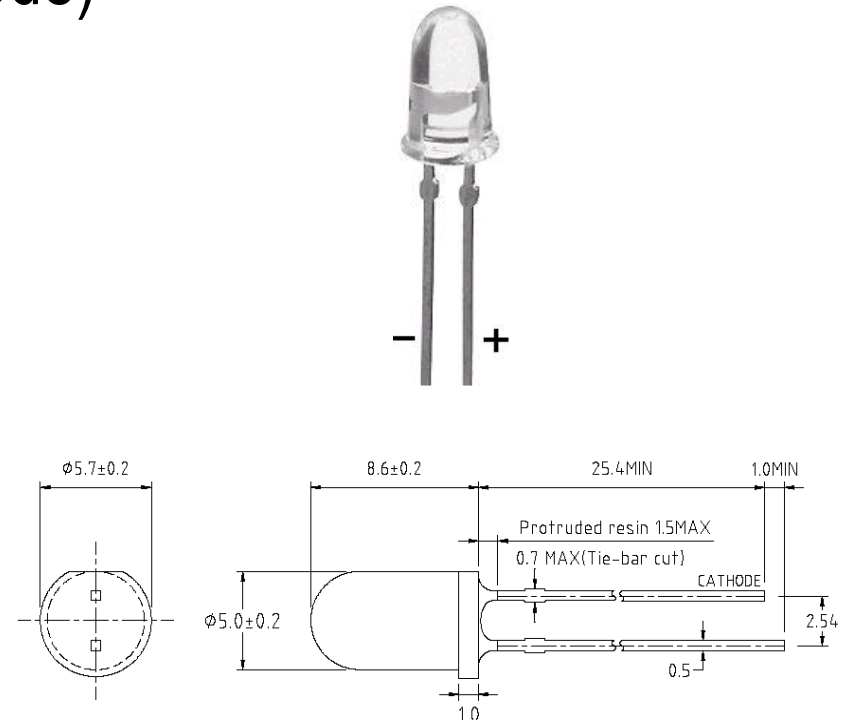
## LED (Light Emitting Diode)

- When forward-biased the LED emits light
- The forward voltage is different for different colours, generally forward voltages of LEDs are higher than in normal diodes
- Light intensity is different for different colours



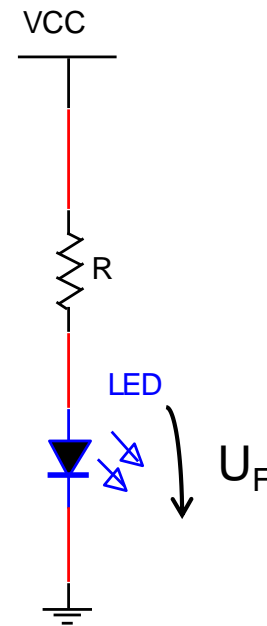
## LED Biasing

- The current of a LED is limited by a resistor.
- Forward voltage as well as the recommend forward current shall be checked from the data sheet of LED.
- $U_{CC} = R I_{LED} + U_F$




## STUDY MATERIAL

	Wavelength (nm)	Color Name	Fwd Voltage (Vf @ 20mA)	Intensity 5mm LEDs	Viewing Angle	LED Dye Material
	940	Infrared	1.5	16mW @50mA	15°	GaAlAs/GaAs - Gallium Aluminum Arsenide/Gallium Arsenide
	880	Infrared	1.7	18mW @50mA	15°	GaAlAs/GaAs - Gallium Aluminum Arsenide/Gallium Arsenide
	850	Infrared	1.7	26mW @50mA	15°	GaAlAs/GaAs - Gallium Aluminum Arsenide/Gallium Arsenide
	660	Ultra Red	1.8	2000mcd @50mA	15°	GaAlAs/GaAs - Gallium Aluminum Arsenide/Gallium Aluminum Arsenide
	635	High Eff. Red	2.0	200mcd @20mA	15°	GaAsP/GaP - Gallium Arsenic Phosphide / Gallium Phosphide
	633	Super Red	2.2	3500mcd @20mA	15°	InGaAlP - Indium Gallium Aluminum Phosphide
	620	Super Orange	2.2	4500mcd @20mA	15°	InGaAlP - Indium Gallium Aluminum Phosphide
	612	Super Orange	2.2	6500mcd @20mA	15°	InGaAlP - Indium Gallium Aluminum Phosphide
	605	Orange	2.1	160mcd @20mA	15°	GaAsP/GaP - Gallium Arsenic Phosphide / Gallium Phosphide
	595	Super Yellow	2.2	5500mcd @20mA	15°	InGaAlP - Indium Gallium Aluminum Phosphide
	592	Super Pure Yellow	2.1	7000mcd @20mA	15°	InGaAlP - Indium Gallium Aluminum Phosphide
	585	Yellow	2.1	100mcd @20mA	15°	GaAsP/GaP - Gallium Arsenic Phosphide / Gallium Phosphide
	574	Super Lime Yellow	2.4	1000mcd @20mA	15°	InGaAlP - Indium Gallium Aluminum Phosphide
	570	Super Lime Green	2.0	1000mcd @20mA	15°	InGaAlP - Indium Gallium Aluminum Phosphide
	565	High Efficiency Green	2.1	200mcd @20mA	15°	GaP/GaP - Gallium Phosphide/Gallium Phosphide
	560	Super Pure Green	2.1	350mcd @20mA	15°	InGaAlP - Indium Gallium Aluminum Phosphide
	555	Pure Green	2.1	80mcd @20mA	15°	GaP/GaP - Gallium Phosphide/ Gallium Phosphide
	525	Aqua Green	3.5	10,000mcd @20mA	15°	SiC/GaN - Silicon Carbide / Gallium Nitride
	505	Blue Green	3.5	2000mcd @20mA	45°	SiC/GaN - Silicon Carbide / Gallium Nitride
	470	Super Blue	3.6	3000mcd @20mA	15°	SiC/GaN - Silicon Carbide / Gallium Nitride
	430	Ultra Blue	3.8	100mcd @20mA	15°	SiC/GaN - Silicon Carbide / Gallium Nitride

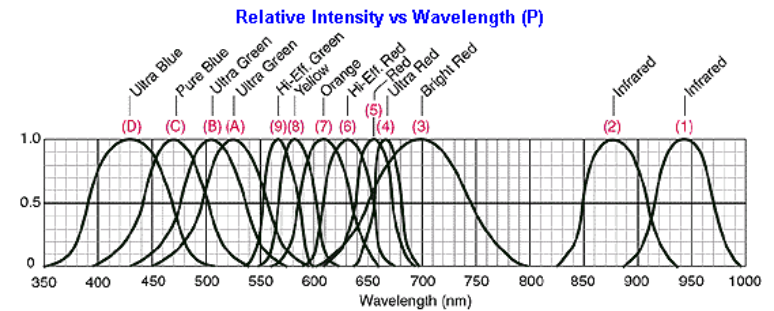


Forward Current vs Forward Voltage

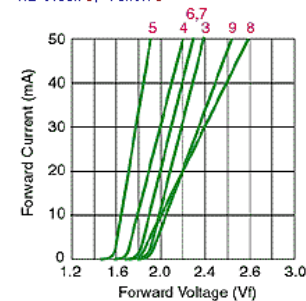Red 5, Ultra Red 4, HE Red 6, Orange 7, Bright Red 3, HE Green 9, Yellow 8



Relative Luminous Intensity vs Forward Current

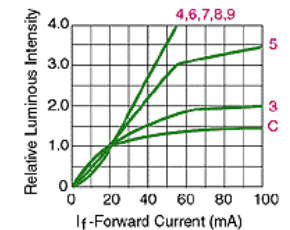Ultra Red 4, HE Red 6, Orange 7, Yellow 8, HE Green 9, Red 5, Bright Red 3, Pure Blue C





## STUDY MATERIAL



# Photodiode

- Light is changed as current in a photodiode

- It is used as reverse-biased

- This structure is most commonly fabricated in a lightly to moderately doped, 200-500  $\mu\text{m}$  thick, n-type silicon substrate. The front of the wafer is heavily doped with a p-type dopant, like Boron, by ion implantation, in such a way as to produce a shallow junction. The rear of the wafer is heavily doped with an n-type dopant, such as Phosphorous, by ion implantation for better ohmic contact. The contact oxide by thermal oxidation is the window allowing incident light in, while passivating the silicon surface.

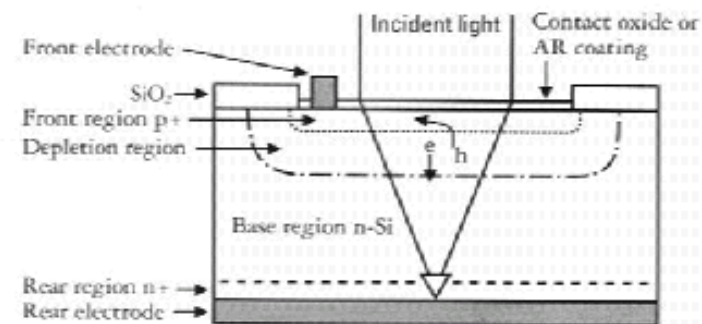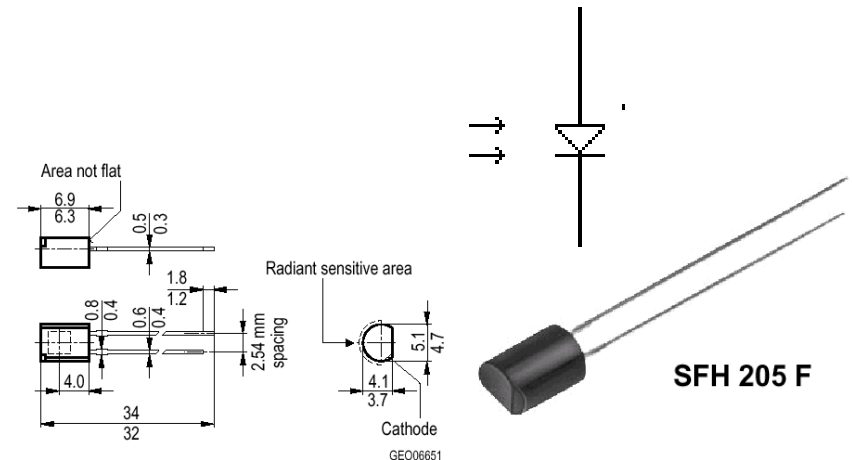
- When the energy of photon,  $h\nu$ , is larger than the forbidden gap of silicon, 1.12 eV (equivalent to about 1100 nm in wavelength), the absorbed photon may excite an electron from valence band to conduction band and leave a hole in valence band, in other words, generating an electron-hole pair.



# Sensitivity of Example Photodiode


Relative spectral sensitivity

$$S_{\text{rel}} = f(\lambda)$$

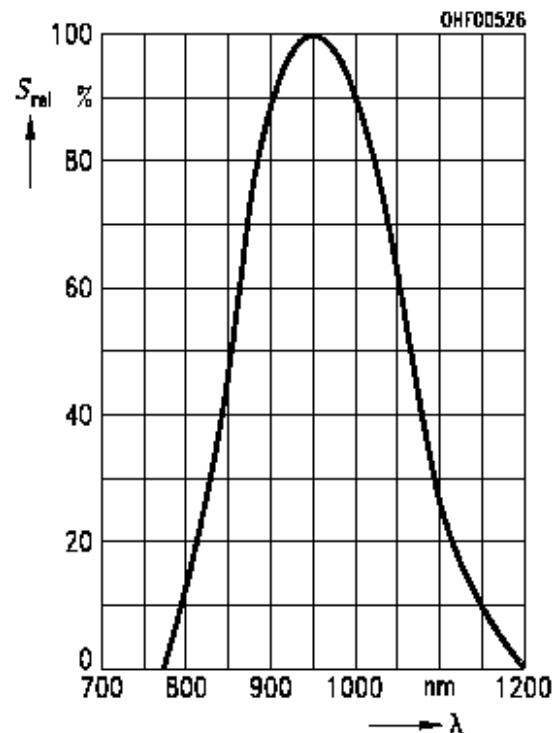

Photocurrent  $I_P = f(E_e)$ ,  $V_R = 5 \text{ V}$

Open-circuit voltage  $V_O = f(E_e)$

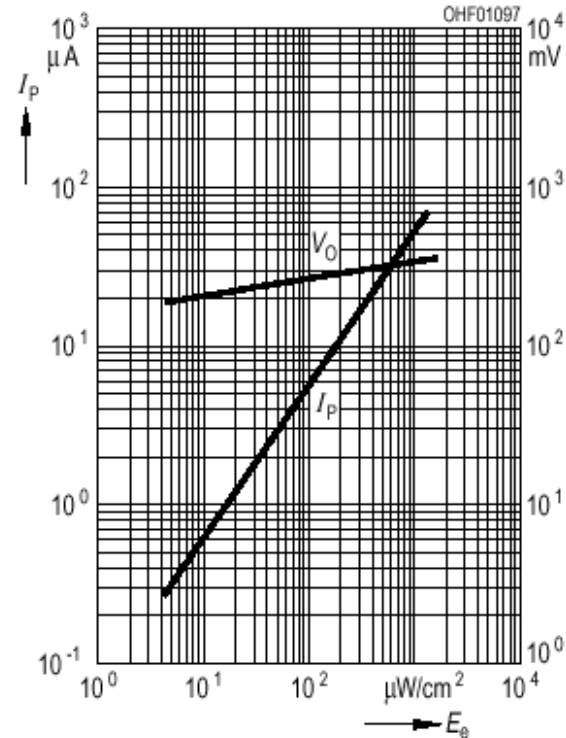




## Dark Current of Example Photodiode


### Dark current

$$I_R = f(V_R), E = 0$$

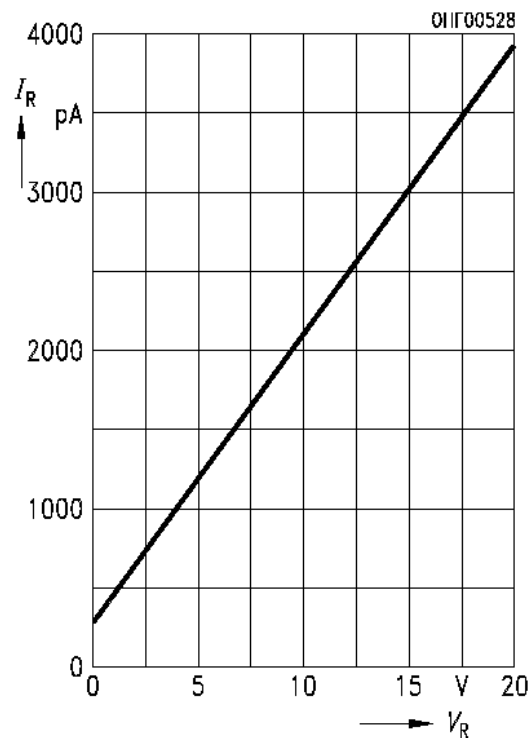
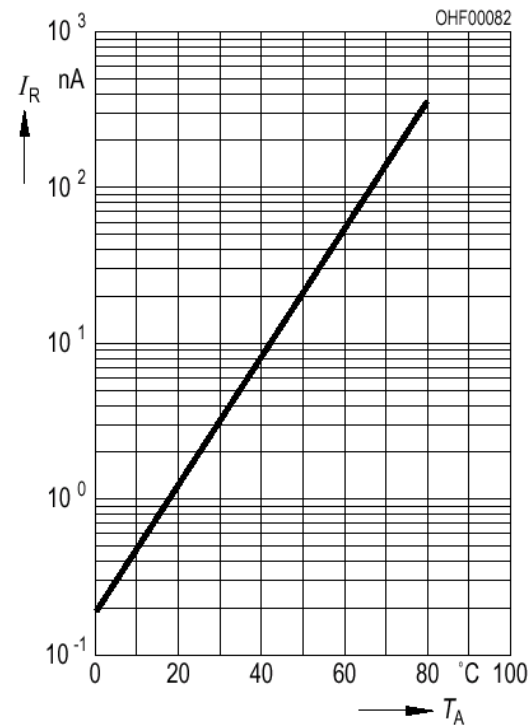
### Dark current

$$I_R = f(T_A), V_R = 10 \text{ V}, E = 0$$



## STUDY MATERIAL



## BJT transistors

## NPN transistor

## PNP transistor


## PINNING

PIN	DESCRIPTION
1	emitter
2	base
3	collector, connected to case

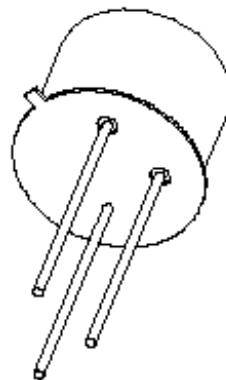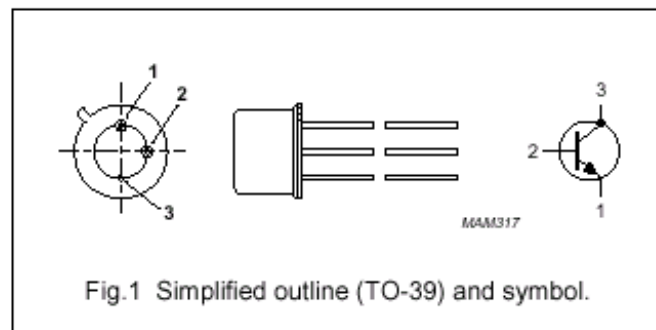


## PINNING

PIN	DESCRIPTION
1	emitter
2	base
3	collector, connected to case

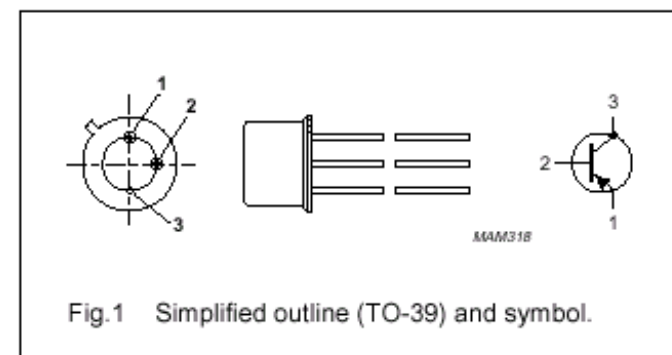

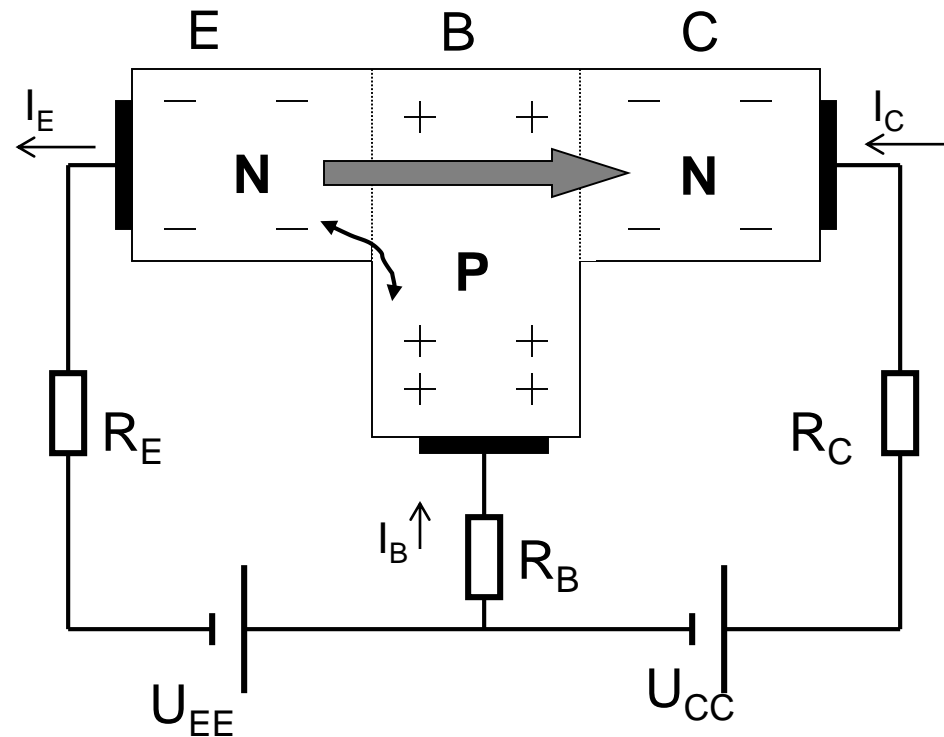
## NPN Transistor

- Because of biasing charge carriers start to recombine at EB junction
- More electrons comes to the emitter from the supply
- Because the base is narrow most of the electrons pass the base to the collector  
=>continuous current flow


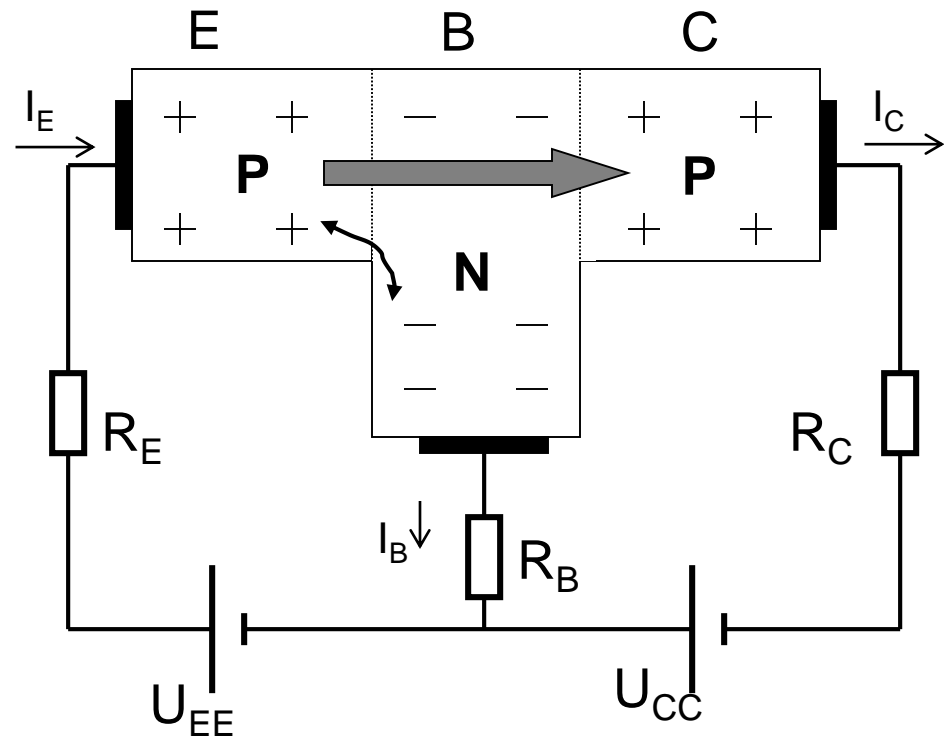
## PNP Transistor

- Because of biasing charge carriers start to recombine at EB junction
- More holes comes to the emitter from the supply
- Because the base is narrow most of the holes pass the base to the collector  
=>continuous current flow



The graph shows the relationship between collector current  $I_C$  and collector-emitter voltage  $V_{CE}$ . A solid line represents the load line, with a dashed extension. The Q-point is marked on the load line. Several curves are plotted, labeled  $I_{B1}$  through  $I_{B5}$  and  $I_{BQ}$ . The Q-point is at  $I_{CQ}$  and  $V_{CEQ}$ . A sinusoidal waveform for  $I_c$  is shown on the  $I_C$  axis, and a sinusoidal waveform for  $V_{ce}$  is shown on the  $V_{CE}$  axis.


## DC Analysis of the BJT Stage

$$I_C = \beta I_B$$


$$I_E = I_C + I_B = (\beta + 1) I_B$$

$$U_{CC} = R_1 I_B + U_{BE} + R_3 I_E$$

$$U_{CC} = R_2 I_C + U_{CE} + R_3 I_E$$

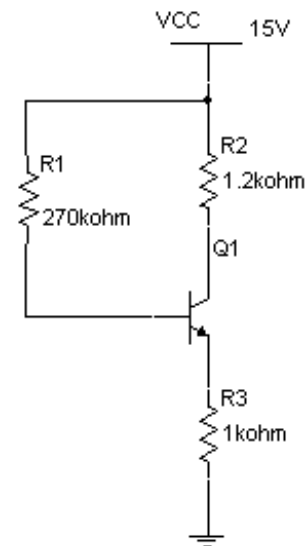

## DC Analysis of the CE BJT Amplifier

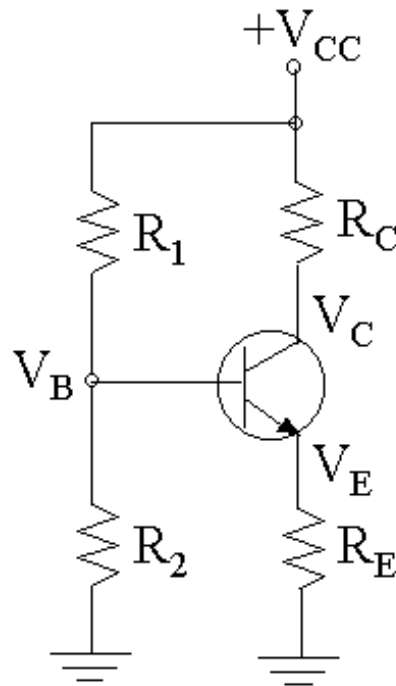

$$V_B = \left( \frac{R_2 // \beta_{DC} R_E}{R_1 + R_2 // \beta_{DC} R_E} \right) V_{CC}$$

If  $\beta_{DC} R_E = R_{IN(base)} \gg R_2$ , then


$$V_B \cong \left( \frac{R_2}{R_1 + R_2} \right) V_{CC}$$

$$V_E = V_B - V_{BE}; \quad I_C \cong I_E = \frac{V_E}{R_E}$$

$$V_C = V_{CC} - I_C R_C$$



## DC Analysis of the CC BJT Amplifier

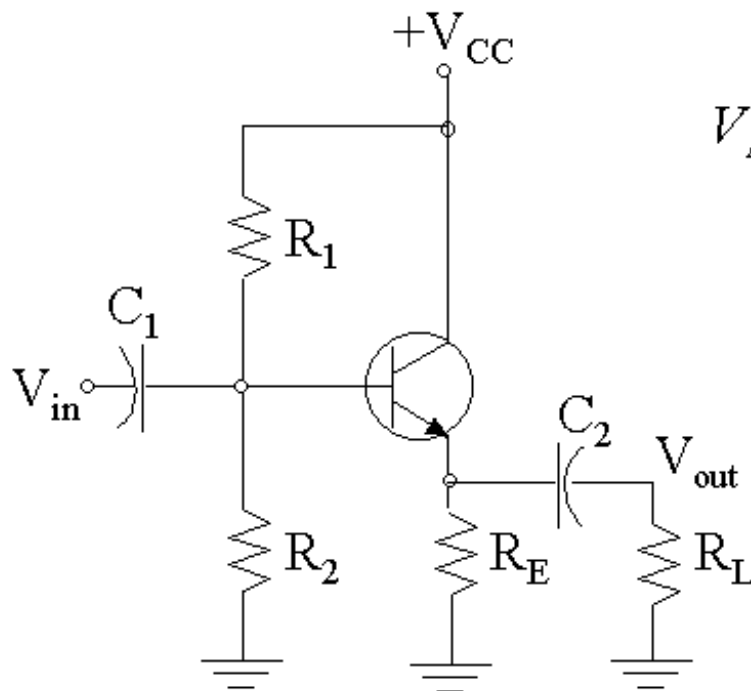

DC analysis:

$$V_B = \left( \frac{R_2 // \beta_{DC} R_E}{R_1 + R_2 // \beta_{DC} R_E} \right) V_{CC}$$

$$V_E = V_B - V_{BE}$$

$$I_E = V_E / R_E$$

$$V_C = V_{CC}$$


The CC amplifier is also known as an emitter-follower since  $V_{out}$  follows  $V_{in}$  in phase and voltage.

## BJT as a Switch

- When output of the gate is high transistor conducts and the LED transmits light. Base resistance is chosen so that the transistor saturates all the current gain values.
- When  $U_o$  is low, the transistor doesn't conduct and no light transmitted

$$-U_o = R_B I_B + U_{BE}$$
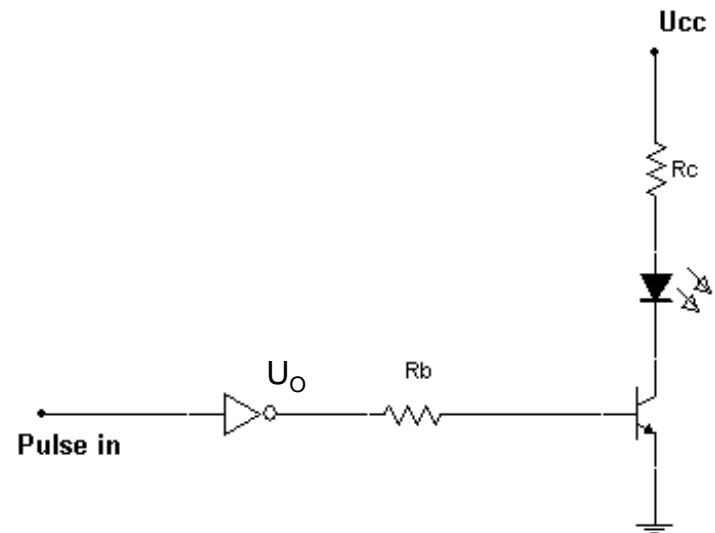
$$-U_{CC} = R_C I_C + U_{CE(sat)} + U_F$$




## BJT Based Relay Control


- When the output of the gate is high, the transistor conducts. The current through the relay coil closes the relay switch and the lamp turns on.
- The diode protects the transistor
- The benefit of the relay in this case is that the high voltage part is totally isolated from the low voltage part.

$$-U_O = R_B I_B + U_{BE}$$
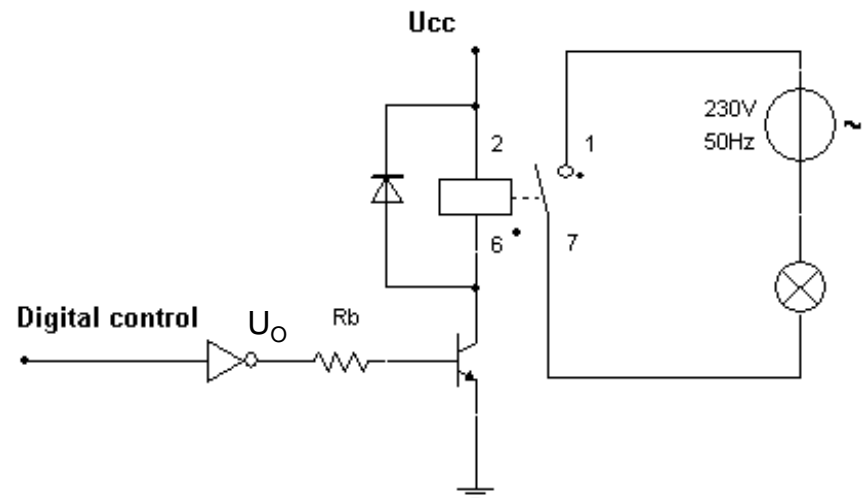
$$-U_{CC} = R_R I_C + U_{CE}(\text{sat})$$




## BJT Based Logic Gate

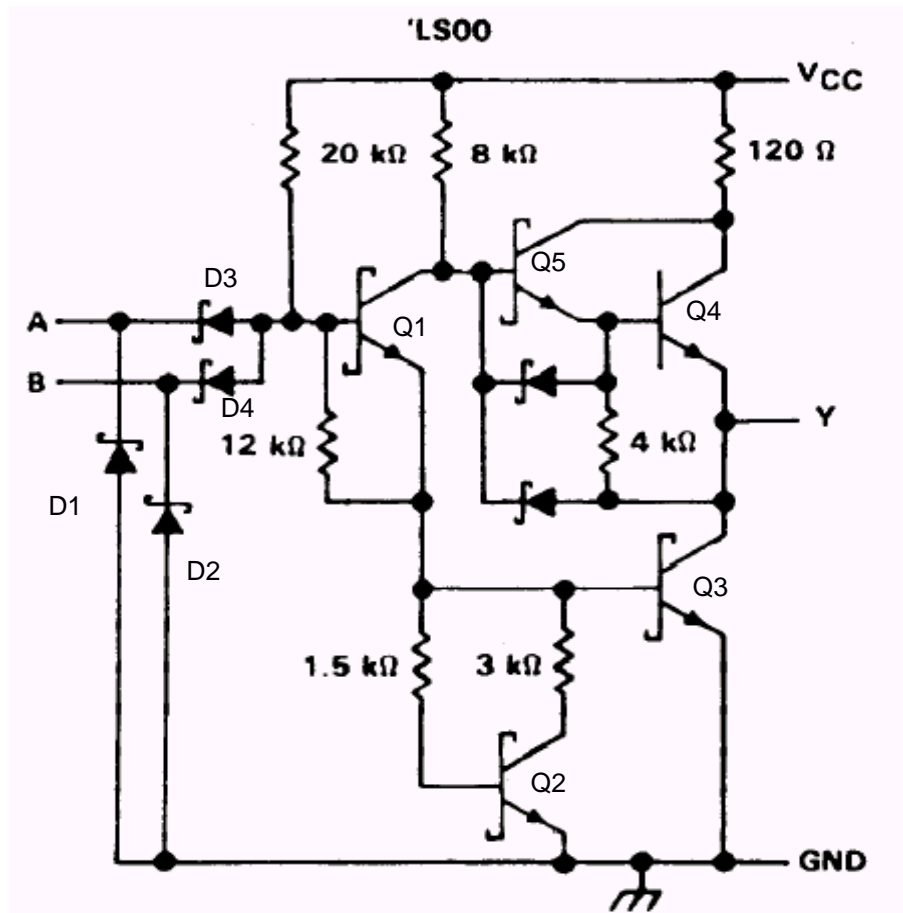


# Field-Effect Transistors


## N-channel JFET

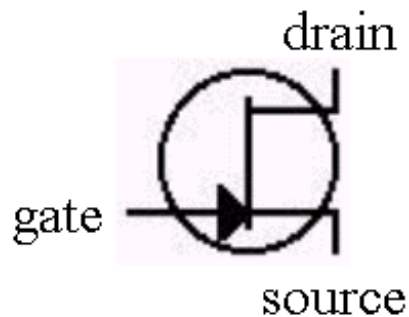

## P-channel JFET

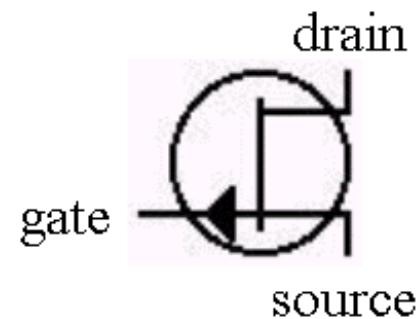




P1086

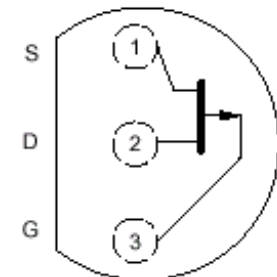TO-226AA  
(TO-92)

Top View

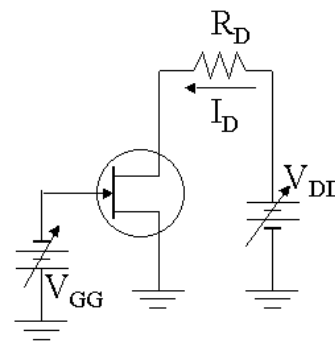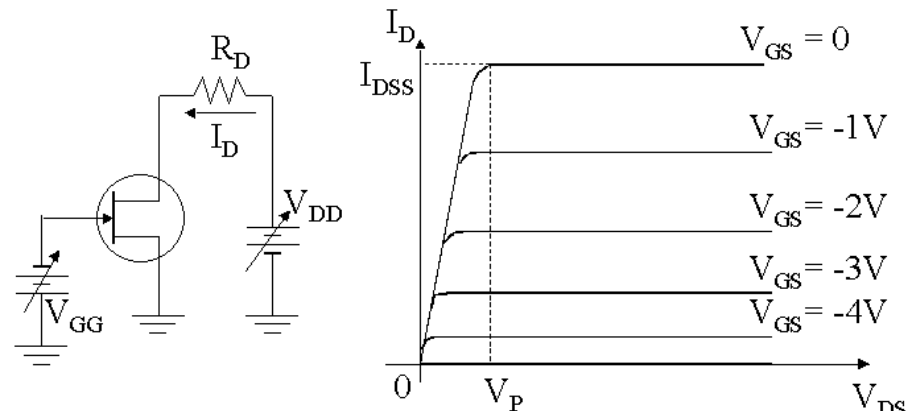
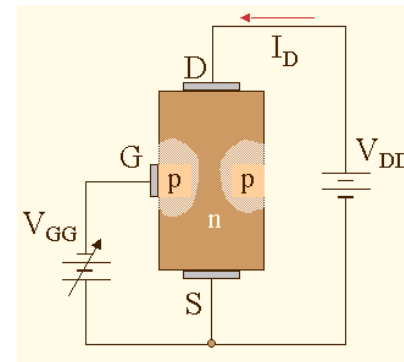
## The Operation of JFET

- By changing the voltage between gate and source terminals the conductivity of channel can be controlled
- Channel off  $\Rightarrow U_{GS} = U_P$
- $U_{GS} = 0 \Rightarrow I_D = I_{DSS}$



## STUDY MATERIAL

## JFET Load Line

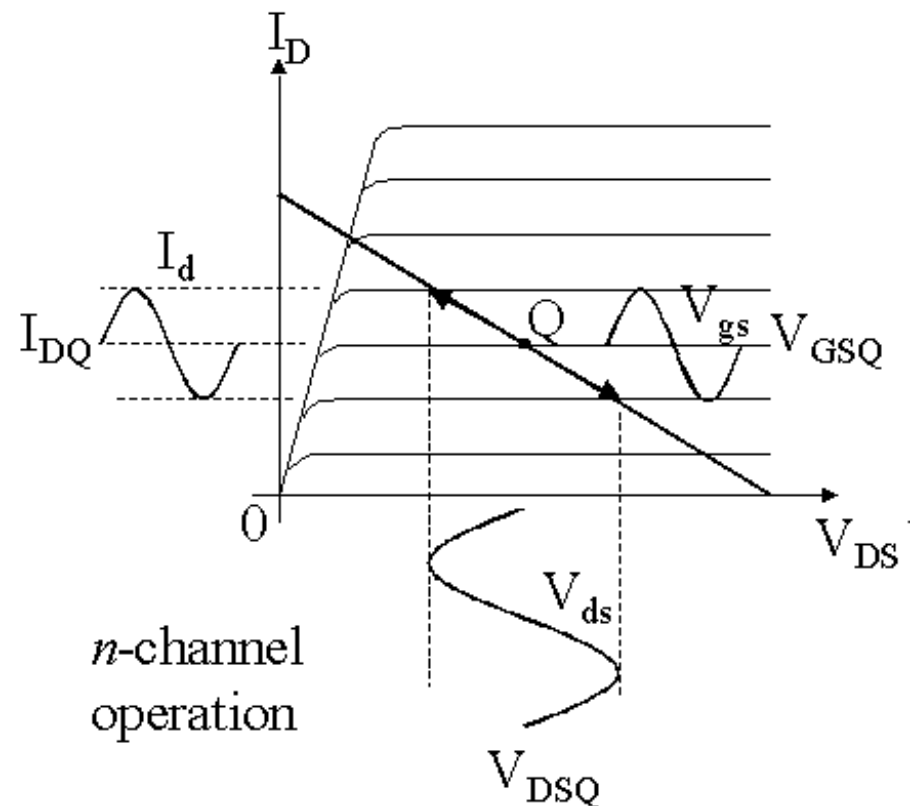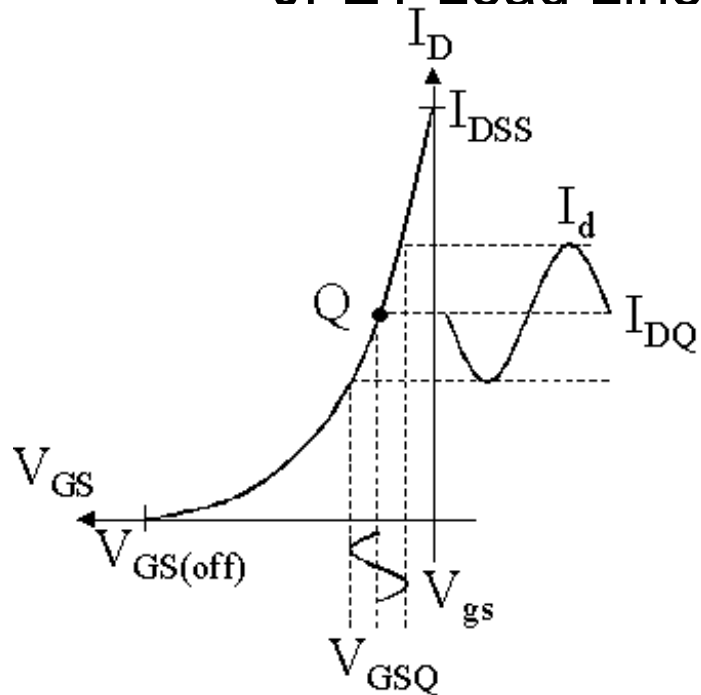




## DC Analysis of the JFET Stage

$$U_G=0, I_G=0$$

$$U_G=U_{GS}+R_S I_D$$


$$I_D=I_{DSS}(1-U_{GS}/U_P)^2$$

$$U_{DD}=R_D I_D+U_{DS}+R_S I_D$$

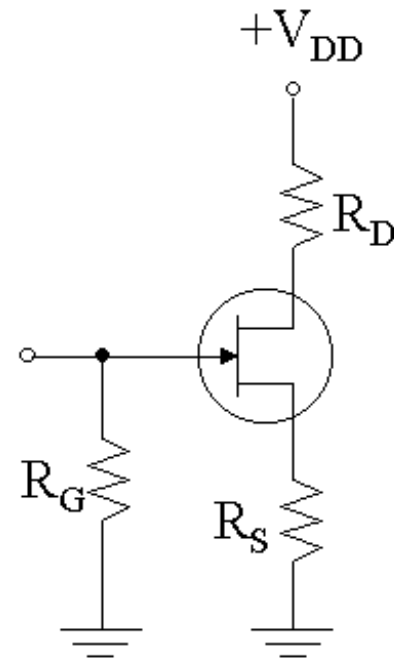


## Field-Effect Transistors

N-channel depletion  
type MOSFET

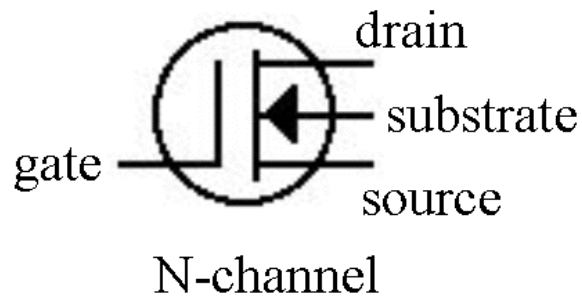

P-channel depletion type  
MOSFET




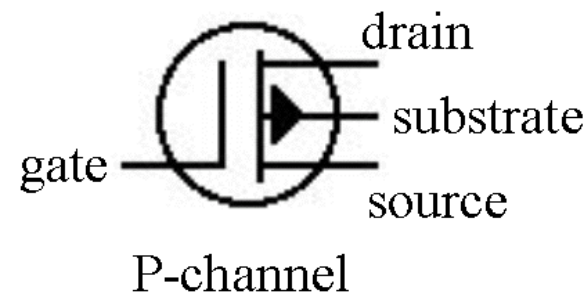


## STUDY MATERIAL

## Field-Effect Transistors

N-channel enhancement  
type MOSFET

P-channel enhancement  
type MOSFET

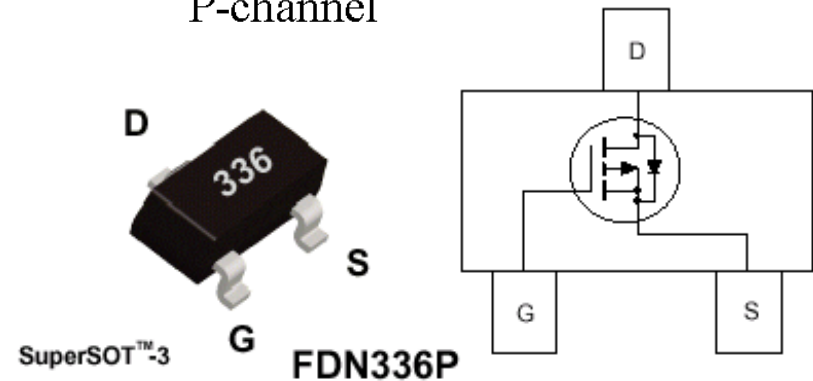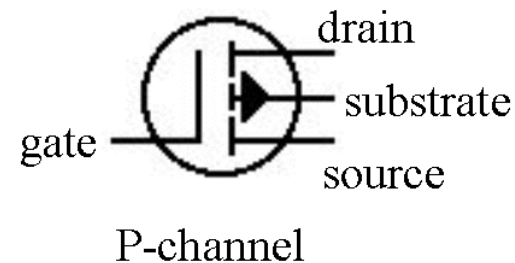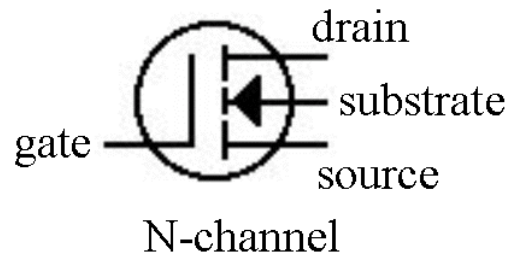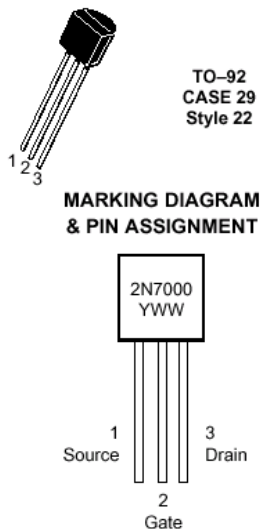


## DC Analysis Of the Enhancement-type Mosfet

$$I_D = 0.5 \mu_n C_{OX} (W/L) (U_{GS} - U_T)^2$$







$$I_D = K (U_{GS} - U_T)^2$$

$$U_{R2} = U_{GS} = R_2 U_{DD} / (R_1 + R_2)$$

$$U_{DD} = R_D I_D + U_{DS}$$

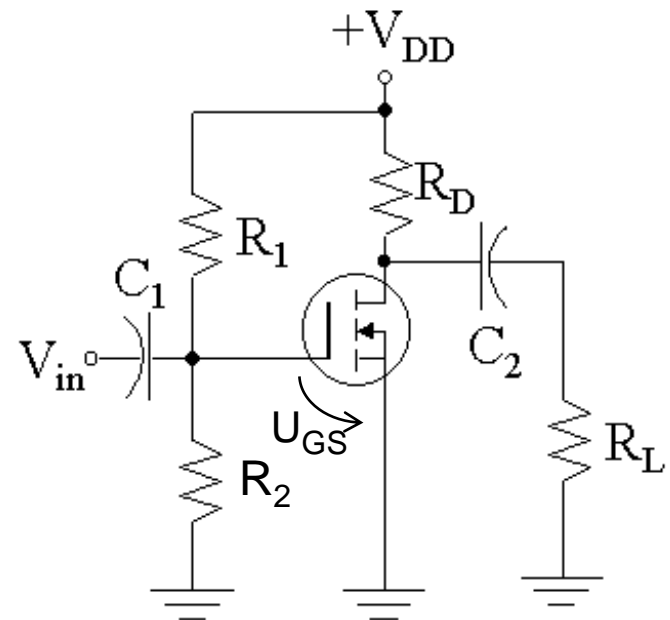

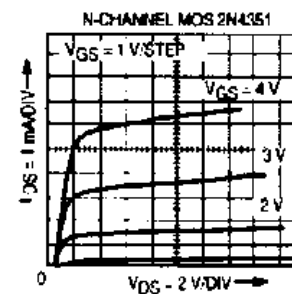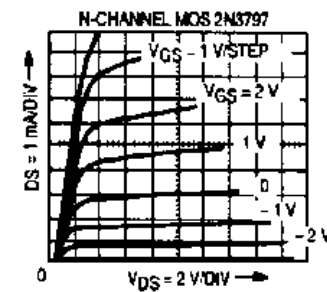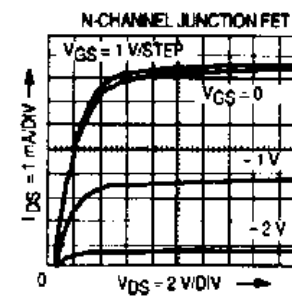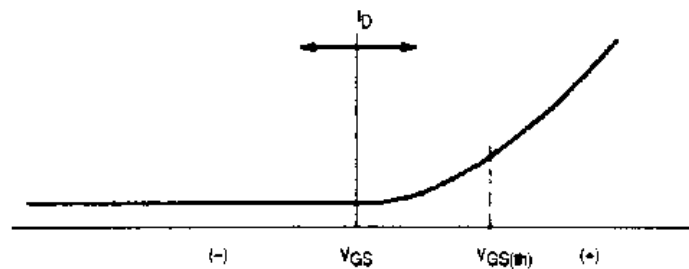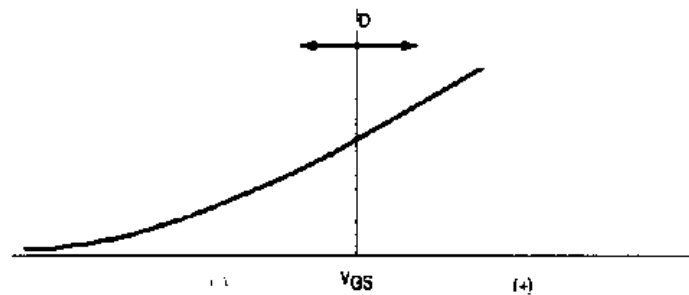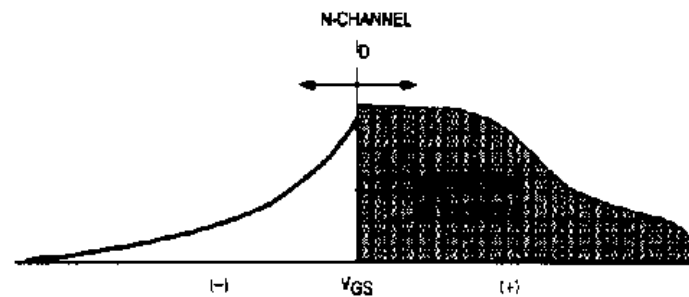
# $f(U_{GS}, I_D)$ for Different FET Types




## MOSFET as a Switch

- If A is high M1 conducts and the output Y is low
- If A is low M2 conducts and the output Y is high

=> Inverter

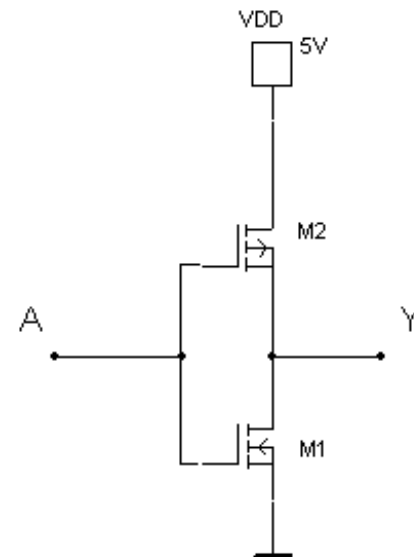

# CMOS NAND

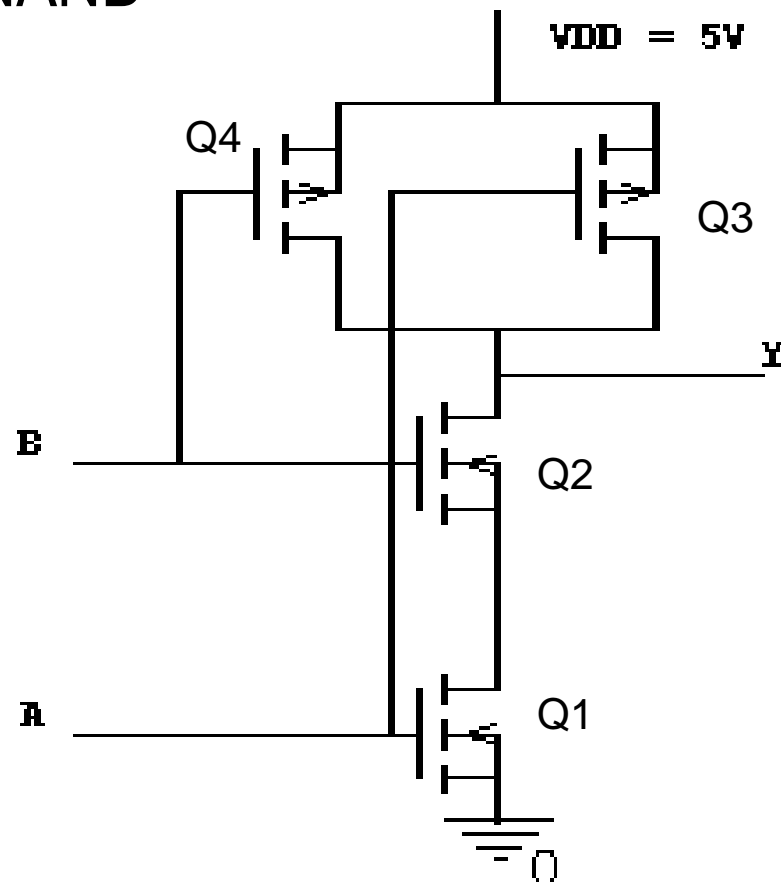



# Operational Amplifiers

Ideal operational amplifier

Inverting configuration

Non-inverting configuration


Buffer amplifier

Summer


Differential amplifier

## LM741 Operational Amplifier

Metal Can Package

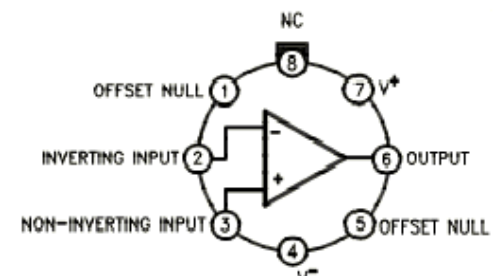

Dual-In-Line or S.O. Package

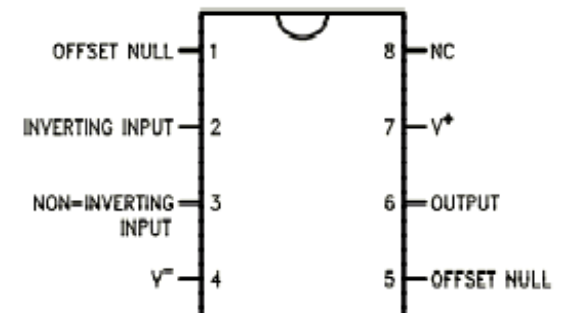

## An Ideal Op Amp


$$A \gg$$

$$Z_i \gg$$

$$Z_o \ll$$

$$u_o = A(u_+ - u_-)$$

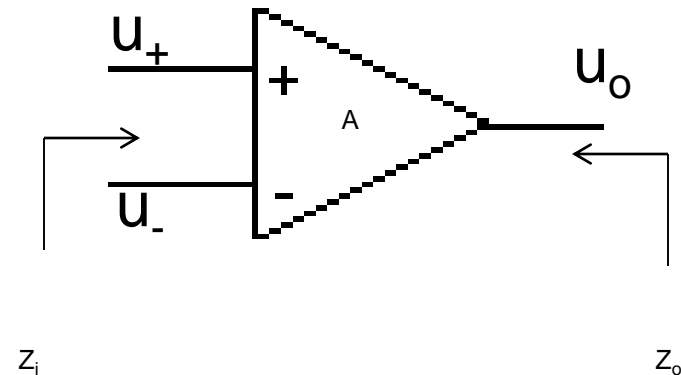If  $A \gg$ ,  $u_+ = u_-$ , virtual short-circuit




## Inverting Configuration

$$u_+ = 0$$

$$u_- = u_o R_1 / (R_1 + R_2) + u_i R_2 / (R_1 + R_2)$$

If  $A \gg 1$ , then  $u_+ = u_-$

$$u_o = -u_i R_2 / R_1$$

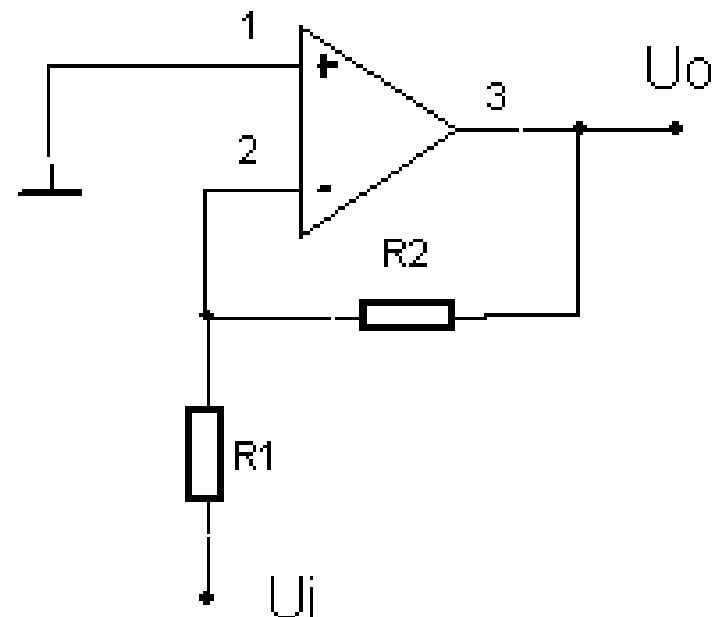


## Non-inverting Configuration

$$u_+ = u_i$$

$$u_- = u_o R_1 / (R_1 + R_2)$$

If  $A \gg 1$ , then  $u_+ = u_-$

$$u_o = (R_1 + R_2) u_i / R_1$$

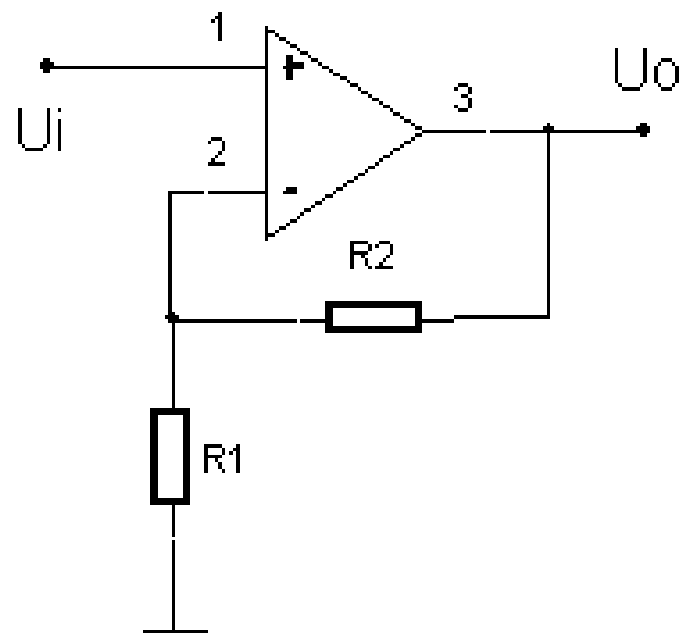


## Buffer Amplifier

$$u_+ = u_i$$


$$u_- = u_o$$

If  $A \gg 1$ , then  $u_o = u_i$

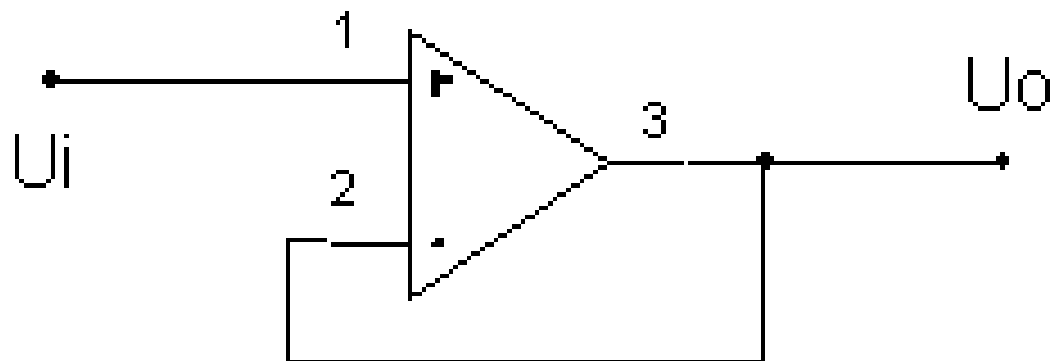
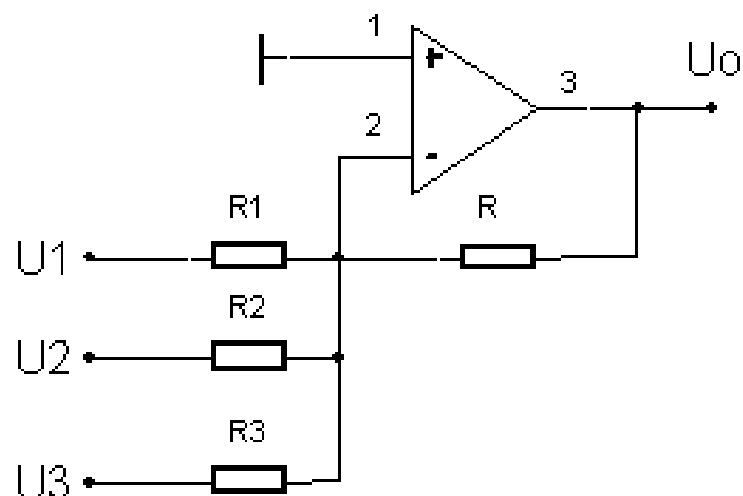
## Summer (inverting)

$$u_o = -(Ru_1/R_1 + Ru_2/R_2 + Ru_3/R_3)$$




## Differential Amplifier

- If the resistors are equal, then

$$U_1 - U_2$$

$$U_o =$$

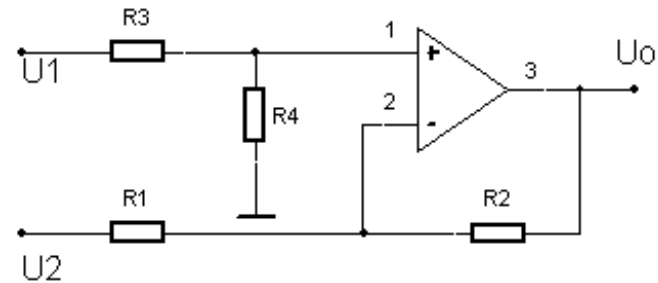




# Power Semiconductors


4-layer diode

Thyristor

PIN CONFIGURATION

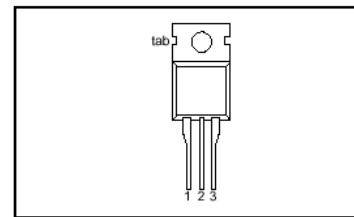

SYMBOL

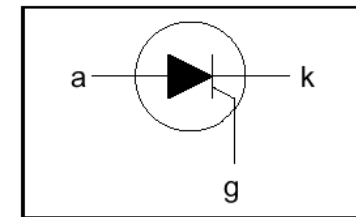

PINNING - TO220AB


PIN	DESCRIPTION
1	cathode
2	anode
3	gate
tab	anode

**BT151 series**


# Power Semiconductors

## Diac

OUTLINE - SOD27

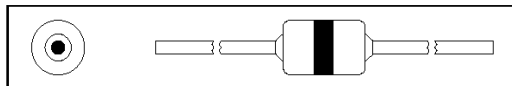


SYMBOL

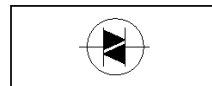


**BR100/03**

## Triac

PIN CONFIGURATION

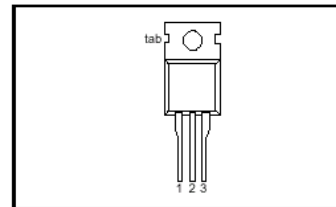

SYMBOL

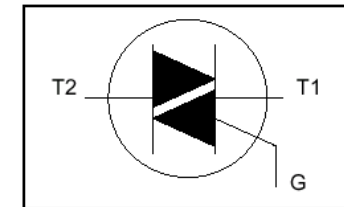

PINNING - TO220AB

PIN	DESCRIPTION
1	main terminal 1
2	main terminal 2
3	gate
tab	main terminal 2

**BT138 series**

## Dimmer Circuit

