```
library ieee;
use ieee.std logic 1164.all;
entity ls165 is
      port(PL, CP, CE, DS: in std logic;
      D: in std logic vector(0 to 7);
Q7, Q7INV: out std_logic);
end ls165;
architecture toiminta of ls165 is
begin
       process(CP, CE, PL)
                                 --CP on kello
      variable apu, result: std logic vector(0 to 7);
       begin
             apu:=result; -- := muuttujaan sijoitus
             if(PL='0') then result:=D;
             elsif ((CE='0') and (CP='1' and CP'event)) then
                    for index in 0 to 6 loop
                           result(index+1):=apu(index);
                    end loop;
                    result(0):=DS;
             end if;
             Q7<=result(7);
                                        --kirjoitetaan ulostulo
             Q7INV<= (not result(7));
      end process;
end toiminta;
```

```
--esim2, ls163
library ieee;
use ieee.std logic 1164.all;
entity ls163 is
       port(CLR, LOAD, ENT, ENP, CLK: in std logic;
       D: in std logic vector(3 downto 0); -- A-D
       RCO: out std logic;
Q: out std logic vector(3 downto 0));
end ls163;
architecture toiminta of ls163 is
       function inc counter(input :std logic vector)
       return std logic vector is
               variable result: std_logic_vector(3 downto 0):=input;
               variable carry : std_logic:='1';
               begin
                       for index in 0 to 3 loop
                               result(index):=result(index) xor carry;
                               carry:=input(index) and carry;
                               exit when carry='0';
                       end loop;
               return result;
       end inc counter;
begin
       process(CLK, LOAD, ENT, ENP)
               variable tulos: std_logic_vector(3 downto 0);
       begin
               if(CLK'event and CLK='0') then
   if (CLR='0') then tulos:="0000";
                       elsif(LOAD='0') then tulos:=D;
                       elsif (ENT='1' and ENP='1') then --rivi jatkuu
                               tulos:=inc counter(tulos);
                       end if;
               end if;
               Q<=tulos;
               if (tulos="1111") then RCO<='1';
               else RCO<='0';
               end if;
       end process;
end toiminta;
```