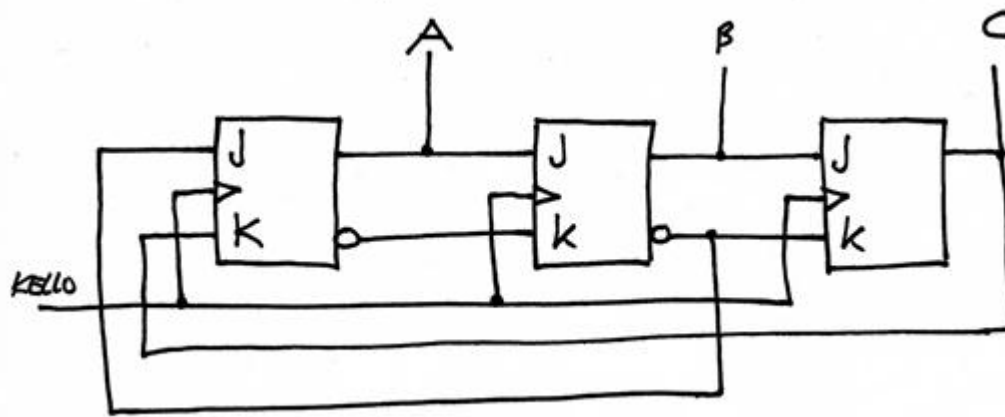


Exercise 7

- Find the state diagram of the circuit below.



- Design a sequential circuit that fulfills the following state diagram.

