

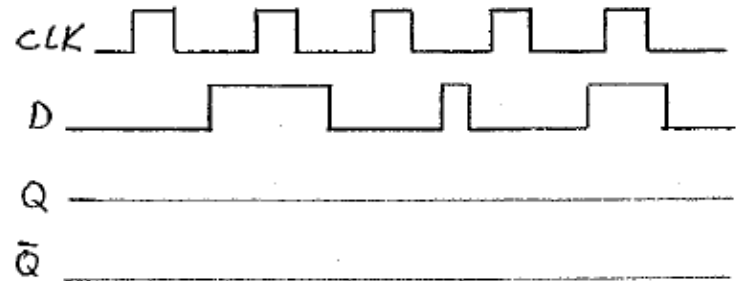
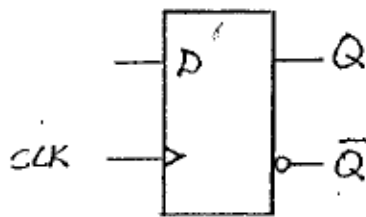


Exercise 2


1. Draw the outputs

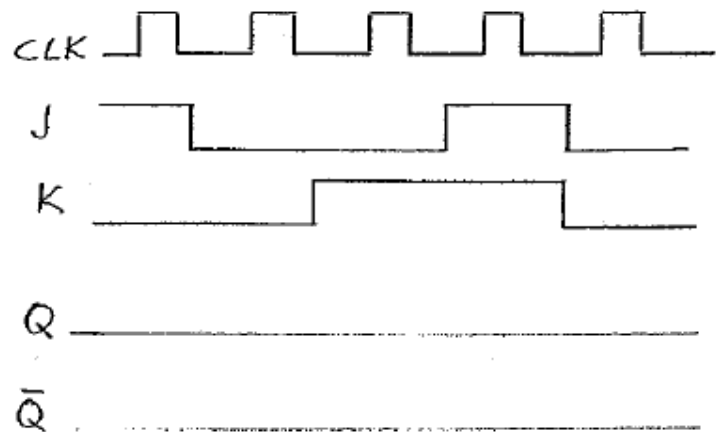

2. Draw the outputs

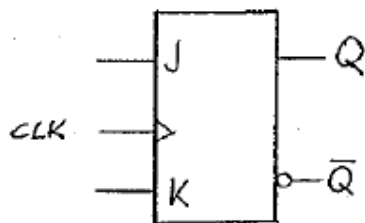

3. Draw Q_A and Q_B .

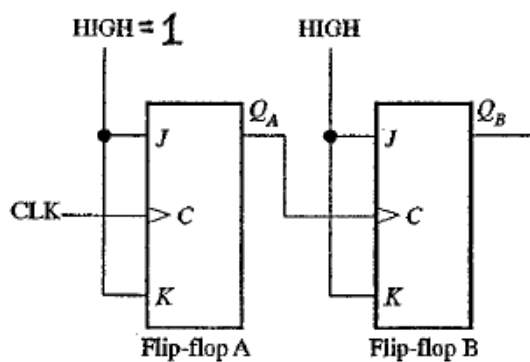

4. Draw data output.

