

Exercise 1

1. Simplify following Boolean functions
 - a. $Y = A\bar{B}\bar{C}\bar{D} + \bar{A}BD + \bar{B}C\bar{D} + \bar{A}\bar{B}\bar{D} + ABD$
 - b. $W = \overline{D(A + \bar{B} + C)} + \overline{C(A + \bar{B}\bar{D})} + A\bar{B}\bar{C}\bar{D}$
 - c. $W = \overline{\bar{C}(\bar{A} + \bar{B})(C + \bar{B}\bar{D}(A + \bar{B}))}$
2. Make the truth table for $Y = A\bar{B}\bar{C}\bar{D} + \bar{A}BD + \bar{B}C\bar{D} + \bar{A}\bar{B}\bar{D} + ABD$ and form the Carnough map. Simplify your map. Sketch a realization of the function Y.
3. Realize the function $Y = A + \bar{B}C$
 - a. By using any type of gates
 - b. By using 2 –input NANDs
 - c. By using a multiplexer
4. Find the logic function of the circuit below.

