
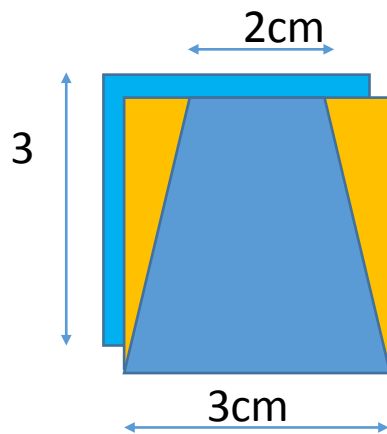


Excercise4

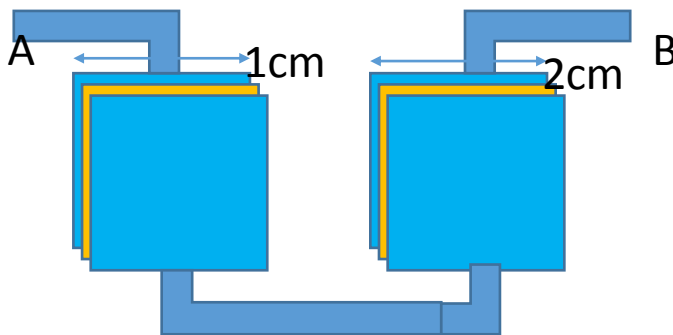- Find the value for the screen printed capacitor below. The permittivity of used dielectric is 3.5 and thickness of dielectric is $3\text{ }\mu\text{m}$.



- You print circuit below by using a screen printer.
 - Draw the circuit diagram of the circuit
 - Find the capacitance between the points A and B if the permittivity of used dielectric is 2.9 and thickness of dielectric is $6\text{ }\mu\text{m}$.



- You use silver ink to print a wire drawn below. The resistivity of ink is $10\text{ }\mu\Omega\text{cm}$ and thickness of wire is $1\text{ }\mu\text{m}$. Calculate the resistance of this wire.

