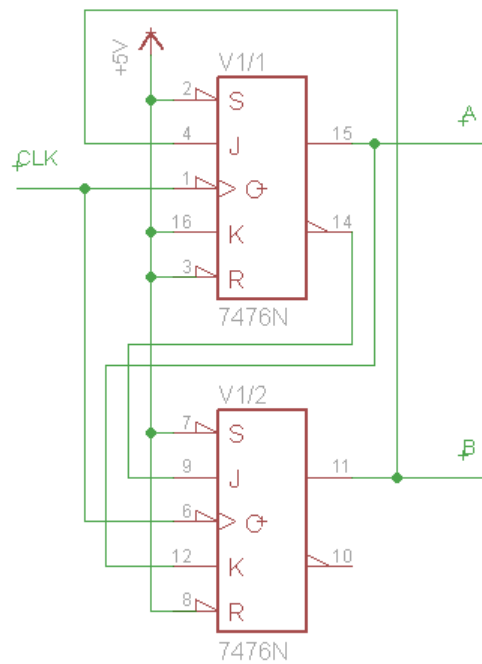


Exercise 6

1. Find the state diagram of the circuit below.



2. Find the state diagram

