
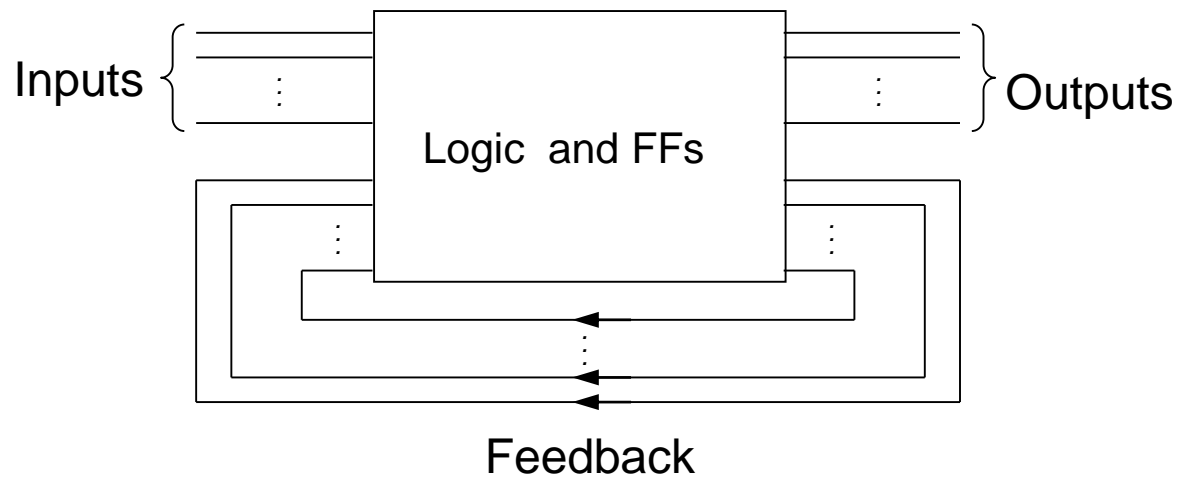



Sequential Logic

 


State Diagram



S R Flip Flop

 


S	R	Q(t+1)
0	0	Q(t)
0	1	0
1	0	1
1	1	X


 


Undefined state


D Flip Flop

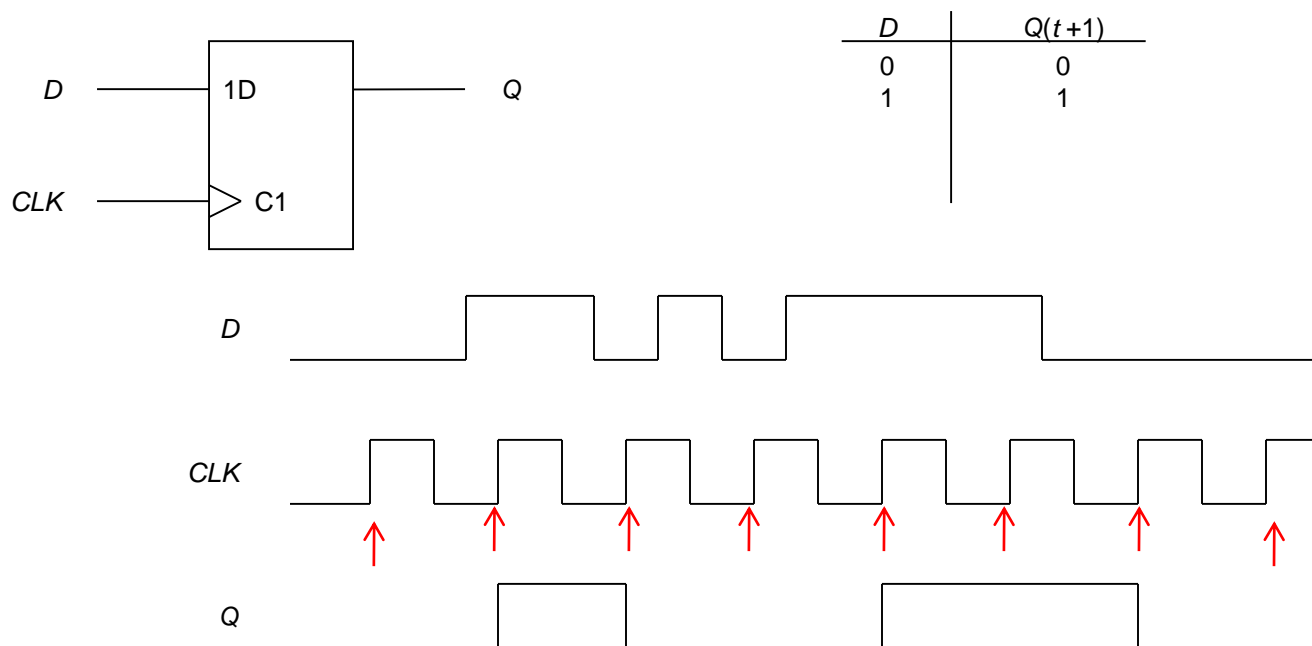

D Latch

  


JK Flip Flop


 


J	K	$Q(t+1)$
0	0	$Q(t)$
0	1	0
1	0	1
1	1	$\overline{Q(t)}$



Q_n	Q_{n+1}	J	K
0	0	0	x
0	1	1	x
1	0	x	1
1	1	x	0

 


PIPO Register

  

SIPO Register

 
 


SIPO Register

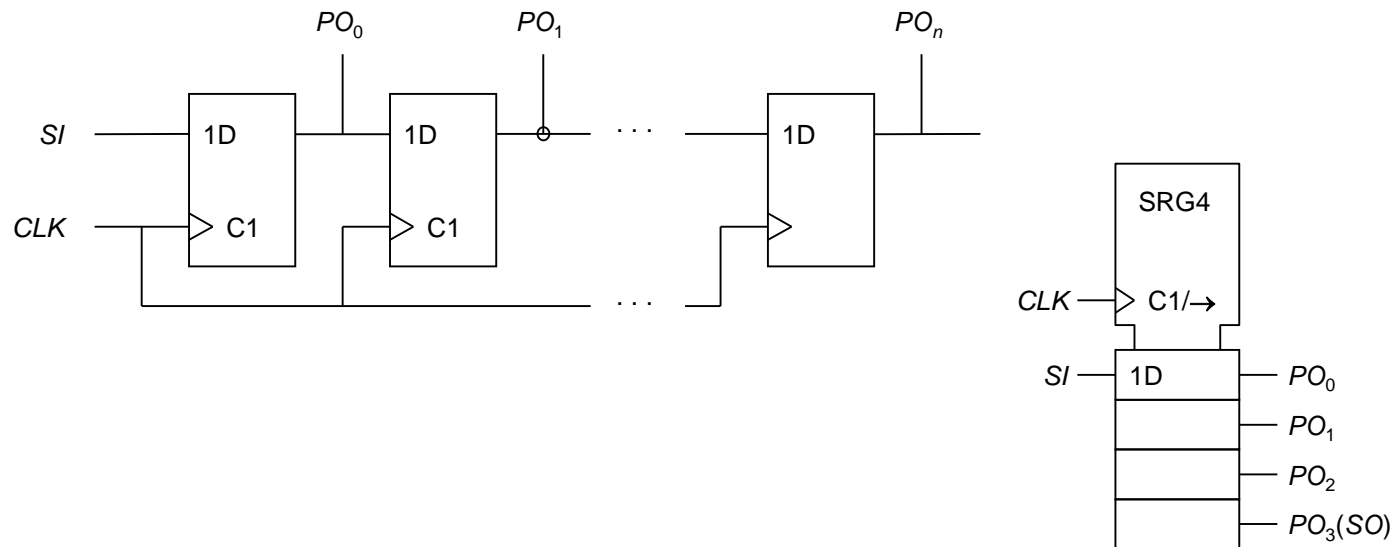

STUDY MATERIAL



Counter

  


The 74LS93A 4-bit binary counter logic diagram. (Pin numbers are in parentheses, and all J and K inputs are internally connected HIGH.)

An Example, Find a State Diagram

Current			Next			Next State		
A	B	C	D _A	D _B	D _C	A	B	C
0	0	0	1	0	0	1	0	0
0	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	1
0	1	1	0	0	1	0	0	1
1	0	0	1	1	0	1	1	0
1	0	1	0	1	0	0	1	0
1	1	0	0	1	1	0	1	1
1	1	1	0	1	1	0	1	1

 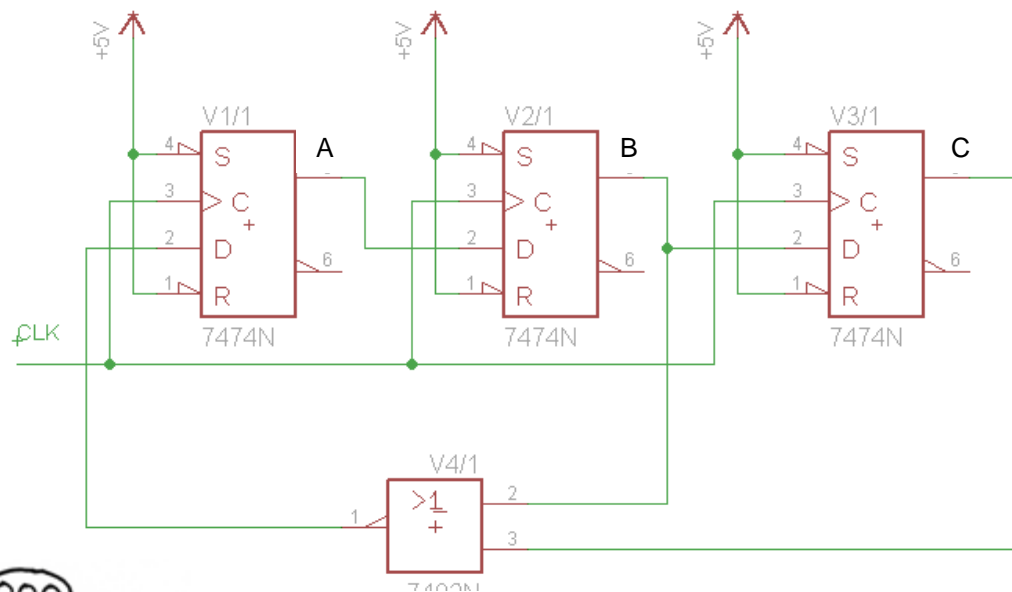

An Example, Design a Circuit

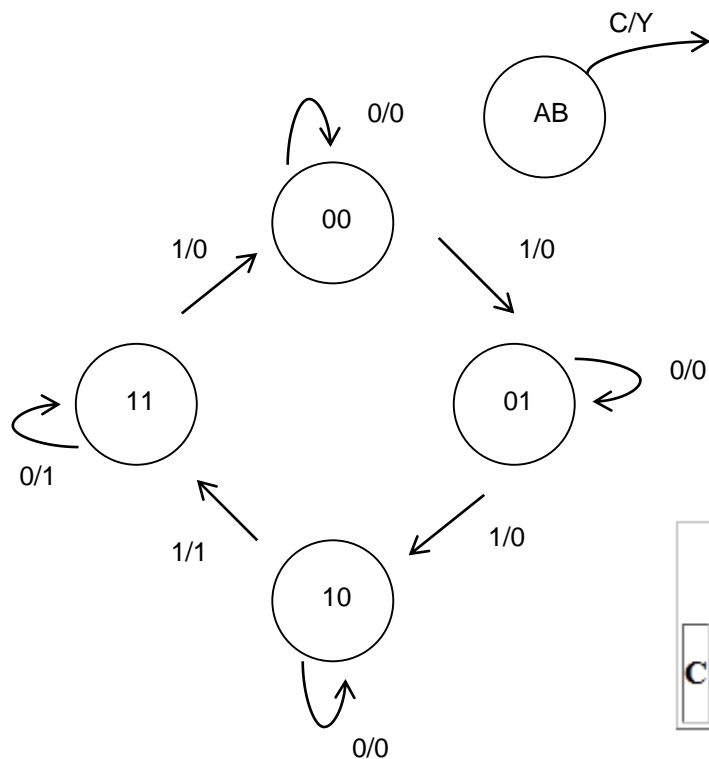

Current st			Next		Next st		Output
A	B	C	Da	Db	A	B	Y
0	0	1	0	1	0	1	0
0	1	1	1	0	1	0	0
1	0	1	1	1	1	1	1
1	1	1	0	0	0	0	0
0	0	0	0	0	0	0	0
0	1	0	0	1	0	1	0
1	0	0	1	0	1	0	0
1	1	0	1	1	1	1	0

Karnaugh Map

		AB			
		00	01	11	10
C	0	0	0	1	1
	1	0	1	0	1

$$Da = A\bar{B} + A\bar{C} + \bar{A}BC$$

Karnaugh Map

		AB			
		00	01	11	10
C	0	0	1	1	0
	1	1	0	0	1

$$Db = B\bar{C} + \bar{B}C$$

STUDY MATERIAL

Example, Circuit Diagram of Design

