


# Boolean Algebra

## Basic operations

- AND ( $AB$ ,  $A$  and  $B$  are Boolean variables)
- OR ( $A+B$ ,  $A$  and  $B$  are Boolean variables)
- NOT ( $\bar{E}$ ,  $E$  is a Boolean variable)


Truth Table of Basic Operations

AND			OR			NOT	
A	B	Y	A	B	Y	A	Y
0	0	0	0	0	0	0	1
0	1	0	0	1	1	1	0
1	0	0	1	0	1		
1	1	1	1	1	1		

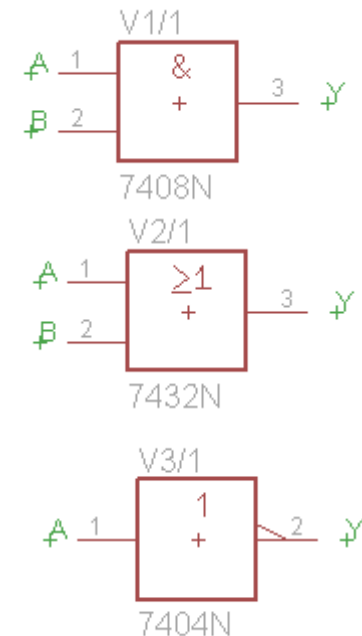


## Some Basic Gates


- OR

 


- NOT

 


- XOR

 




- AND

 

- NAND

 

## Tri State Output

   

## Boolean Algebra Rules

$$A + 0 = A$$

$$A \cdot 1 = A$$

$$A + 1 = 1$$

$$A \cdot 0 = 0$$

$$A + A = A$$

$$A \cdot A = A$$

$$\overline{\overline{A}} = A$$

$$A + \overline{A} = 1$$

$$A \cdot \overline{A} = 0$$

$$A \cdot (\overline{A} + B) = A \cdot B$$

$$A + \overline{A} \cdot B = A + B$$

$$\overline{A + B + C} = \overline{A} \cdot \overline{B} \cdot \overline{C}$$

$$\overline{A \cdot B \cdot C} = \overline{A} + \overline{B} + \overline{C}$$

[http://en.wikipedia.org/wiki/Boolean\\_algebra](http://en.wikipedia.org/wiki/Boolean_algebra)



## Truth Table

- The truth table tells when a given function generates true (=1=H) output value and when false (=0=L) value

### Example Truth Table

- 3 inputs (A, B, C)
- 1 output ( Y )

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

# Carnough Map

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

**Truth Table**

A	B	C	F(ABC)
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

**Karnaugh Map**

		AB			
		00	01	11	10
C	0	0	1	0	0
	1	1	1	0	0

$$F(ABC) = \bar{A}B + \bar{A}C$$

[http://en.wikipedia.org/wiki/Karnaugh\\_map](http://en.wikipedia.org/wiki/Karnaugh_map)

[http://www.ee.calpoly.edu/media/uploads/resources/KarnaughExplorer\\_1.html](http://www.ee.calpoly.edu/media/uploads/resources/KarnaughExplorer_1.html)

## STUDY MATERIAL

## Carnough Map, 4x4

Truth Table

A	B	C	D	F(ABCD)
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	0
1	1	1	1	0

Karnaugh Map

		AB			
		00	01	11	10
CD	00	0	1	1	0
	01	0	1	1	0
	11	1	0	0	1
	10	1	0	0	1

$$F(ABCD) = B\bar{C} + \bar{B}C$$

Truth Table

A	B	C	D	F(ABCD)
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	1
1	1	1	1	0

Karnaugh Map

		AB			
		00	01	11	10
CD	00	1	0	1	1
	01	0	1	0	0
	11	0	0	0	0
	10	1	0	1	1

$$F(ABCD) = A\bar{D} + \bar{B}\bar{D} + \bar{A}B\bar{C}D$$



# Logic Families

Logic family name is related to the transistor technology used inside the circuit (BJTs or MOSFETs or both)

- Bipolar: S, LS, AS, ALS, F, ECL,...
- CMOS: 4000, HC, AC, AHC,...
- Combined: BiCMOS



## Physical Components


**MM**=Manufacturer, SN=Texas Instruments,...

**74** or **54**, 74=commercial, 54=military

**FF**=Family, HC=High-Speed CMOS, LS=Low-power Schottky, LV=Low Voltage,...

**XXX**=Circuit type, 00=NAND, 138=Decoder (3/8),...

**C**=Capsule, N=DIL, D=SOIC,...

 

## Key Electrical Parameters

$U_{OH}$ , Voltage Output High

$U_{OL}$ , Voltage Output Low

$U_{IH}$ , Voltage Input High


$U_{IL}$ , Voltage Input Low

$I_{OH}$ , Current Output High

$I_{OL}$ , Current Output Low

$I_{IH}$ , Current Input High

$I_{IL}$ , Current Input Low

 


Noise Margin

## Example Data of Some Logic Families


Parameter	LS	HC	ABT	Unit
VOH (min)	2.4	4.5	2.5	V
VOL (max)	0.4	0.5	0.5	V
VIH (min)	2	3.5	2	V
VIL(max)	0.8	1.5	0.8	V
IOH(max)	0.4	25.0	15	mA
IOL(max)	16	25.0	20	mA
I <sub>IH</sub> (max)	40	1	1	μA
I <sub>IL</sub> (max)	1600	1	1	μA

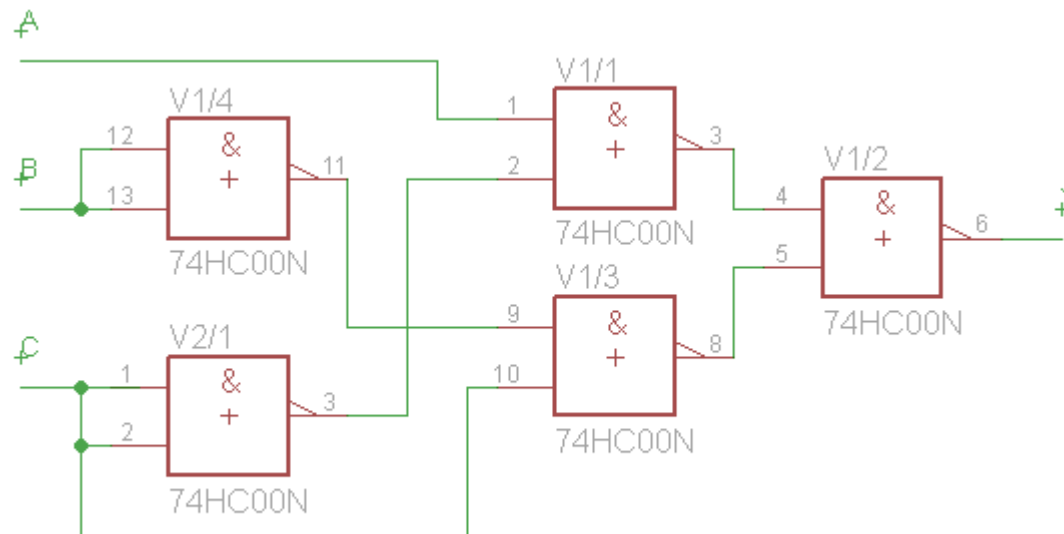Example, Design with 2 input NANDs  $Y = A\bar{C} + \bar{B}C$



## STUDY MATERIAL

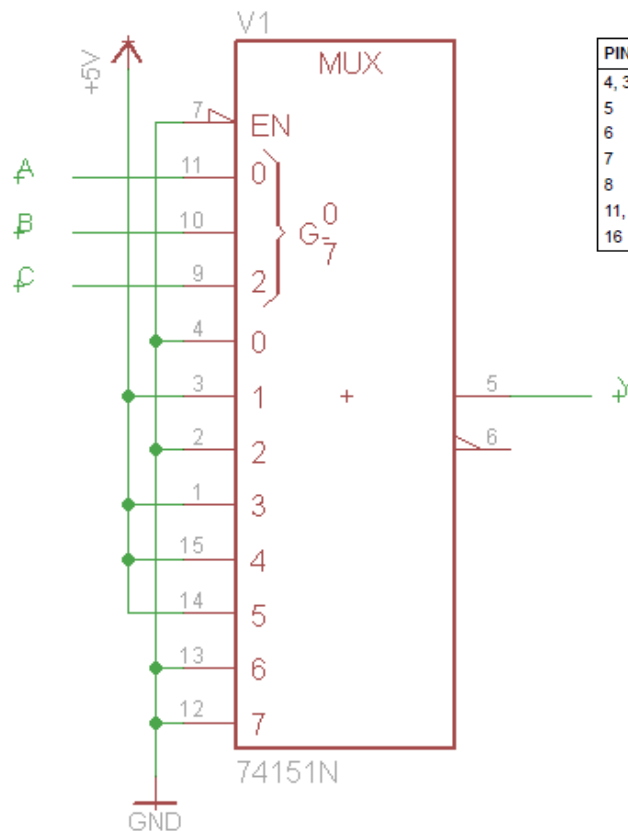Example, Design with Mux,  $Y = A\bar{C} + \bar{B}C$



PIN NO.	SYMBOL	NAME AND FUNCTION
4, 3, 2, 1, 15, 14, 13, 12	$I_0$ to $I_7$	multiplexer inputs
5	$Y$	multiplexer output
6	$\bar{Y}$	complementary multiplexer output
7	$\bar{E}$	enable input (active LOW)
8	GND	ground (0 V)
11, 10, 9	$S_0, S_1, S_2$	select inputs
16	$V_{CC}$	positive supply voltage

FUNCTION TABLE

INPUTS												OUTPUTS	
$\bar{E}$	$S_2$	$S_1$	$S_0$	$I_0$	$I_1$	$I_2$	$I_3$	$I_4$	$I_5$	$I_6$	$I_7$	$\bar{Y}$	$Y$
H	X	X	X	X	X	X	X	X	X	X	X	H	L
L	L	L	L	L	X	X	X	X	X	X	X	H	L
L	L	L	L	H	X	X	X	X	X	X	X	H	L
L	L	L	L	X	H	X	X	X	X	X	X	H	L
L	L	L	L	X	X	H	X	X	X	X	X	H	L
L	L	L	L	X	X	X	H	X	X	X	X	H	L
L	L	L	L	X	X	X	X	H	X	X	X	H	L
L	L	L	L	X	X	X	X	X	H	X	X	H	L
L	L	L	L	X	X	X	X	X	X	H	X	H	L
L	L	L	L	X	X	X	X	X	X	X	H	H	L
L	L	L	L	X	X	X	X	X	X	X	H	H	L
L	L	L	L	X	X	X	X	X	X	X	H	H	L
L	L	L	L	X	X	X	X	X	X	X	H	H	L
L	L	L	L	X	X	X	X	X	X	X	H	H	L
L	L	L	L	X	X	X	X	X	X	X	H	H	L

tes

H = HIGH voltage level

L = LOW voltage level

X = don't care.

